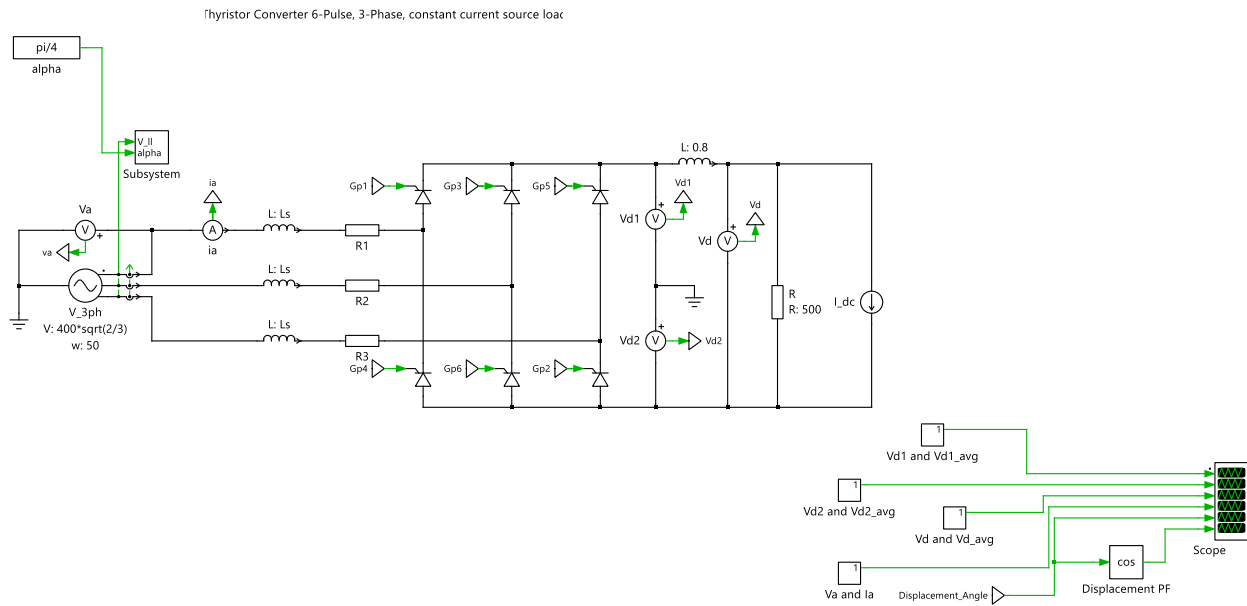


Final Assignment – Converter techniques (cohort 2025-04)


Submitted By: Lokesh Nalla

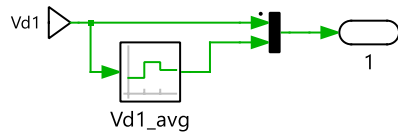Exercise 1: Basic Concepts in 3-Phase Thyristor converters (Thy3_Concepts.plecs)


Simulation Model:



The subsystem of “Vd1 and Vd1_avg” is as below and the same model for other two subsystems: “Vd2 and Vd2_avg, Vd and Vd_avg”.




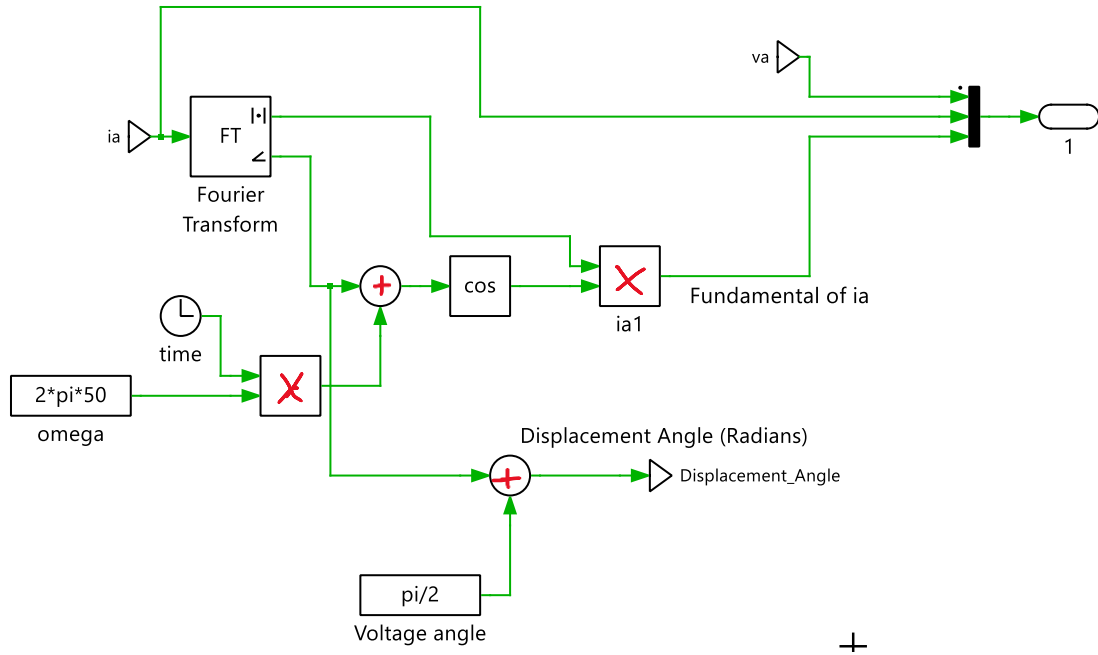The subsystem of “Va and Ia” is as below. Based on FFT, the fundamental component of ‘ia’ is calculated and the same is plotted along with measured ‘va’ and ‘ia’.



Waveforms:

Case 1: Firing angle of 45 degrees

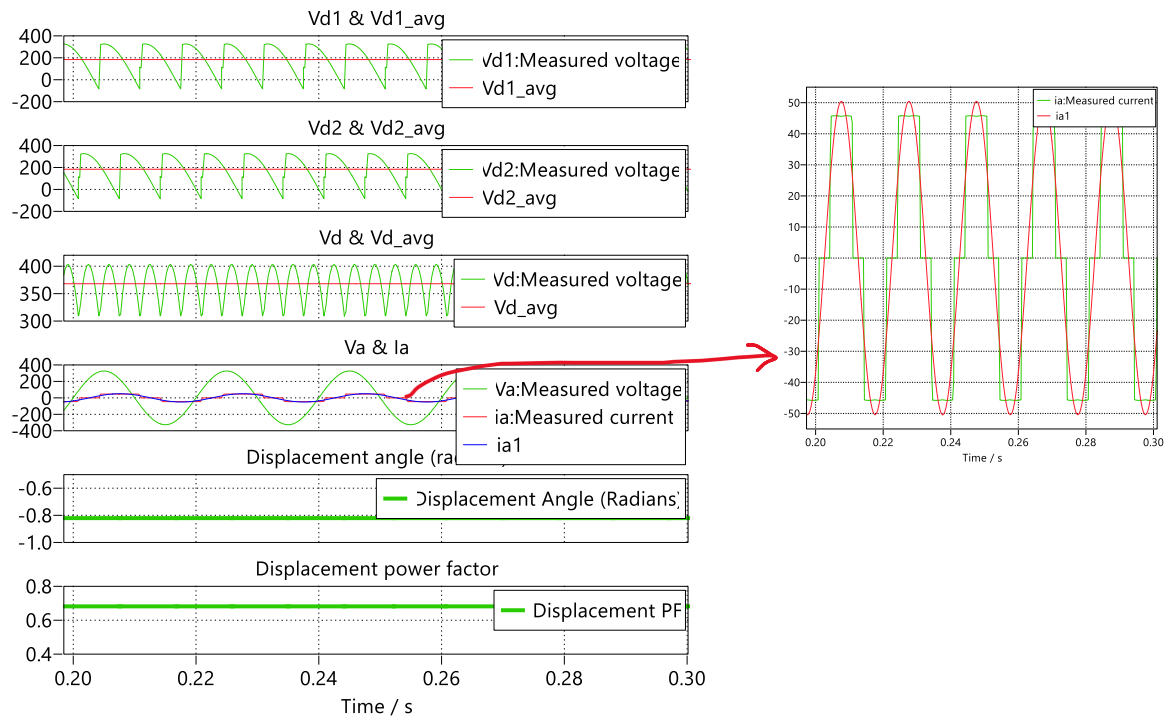

1. Average of Vd1 is 184.052 Volts.
2. Average of Vd2 is 184.051 Volts.
3. Average of Vd is 368.103 Volts.

The average of Vd based on theoretical concept is

$$V_{d_theory} = \left(\frac{3V_{LL,p}}{\pi} \cos \alpha \right) - \left(\frac{3*2\pi*50*L_s}{\pi} + R \right) I_0 = 381.9718 - 13.545 = 368.4268 \text{ Volts.}$$

Therefore, the measured output voltage closely matches with the theoretical output voltage.

4. The measured displacement angle (The phase angle of fundamental current of i_a with respect to v_a) is -0.820638 radians or 47.019 degrees. The measured displacement power factor is 0.68175 lag.

Theoretical Displacement Power Factor (DPF) calculation:

Power Factor (PF) = DPF * Distortion Factor (DF).


$$\text{Where } DF = \frac{I_{a1,rms}}{I_{a,rms}} = \frac{\left(\frac{\sqrt{6}}{\pi} \right) I_{0,dc}}{\left(\frac{\sqrt{2}}{3} \right) I_{0,dc}} = 0.955$$

$$PF = \frac{P}{S} = \frac{V_{d,avg} * I_{0,dc}}{\sqrt{3} V_{LL} I_{a,rms}} = \frac{V_{d,avg} * I_{0,dc}}{V_{LL,p} * I_{0,dc}} = \frac{V_{d,avg}}{V_{LL,p}} = \frac{368.4268}{400 * \sqrt{2}} = 0.6513$$

$$DPF = PF/DF = 0.6513/0.955 = 0.68198 \text{ lag}$$

Therefore the measured DPF is same as with the calculated one.

Case 2: Firing angle of 90 degrees

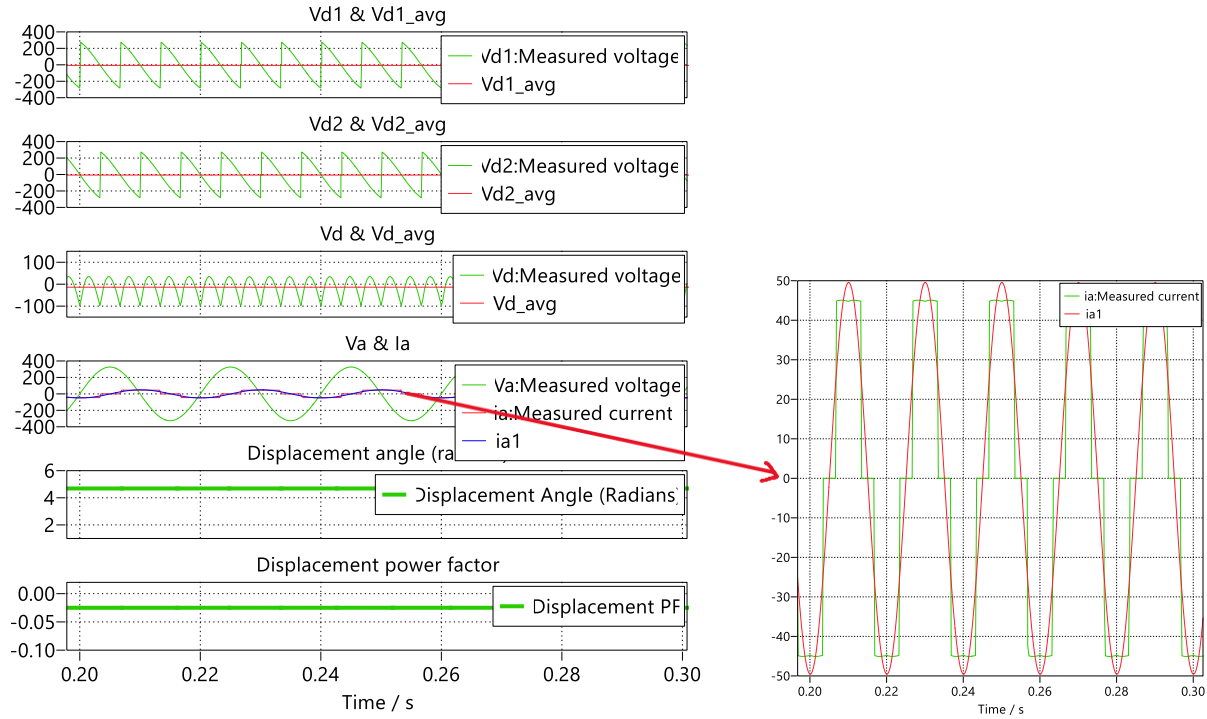

1. Average of Vd1 is -6.83141 Volts.
2. Average of Vd2 is -6.83366 Volts.
3. Average of Vd is -13.6679 Volts.

The average of Vd based on theoretical concept is

$$V_{d_theory} = \left(\frac{3V_{LL,p}}{\pi} \cos \alpha \right) - \left(\frac{3 \cdot 2\pi \cdot 50 \cdot L_s}{\pi} + R \right) I_0 = 0 - 13.545 = -13.545 \text{ Volts.}$$

Therefore, the measured output voltage closely matches with the theoretical output voltage.

4. The measured displacement angle (The phase angle of fundamental current of ia with respect to va) is 4.6874 radians or 268.568 (or 91.432) degrees. The measured displacement power factor is 0.025 lead.

Theoretical Displacement Power Factor (DPF) calculation:

Power Factor (PF) = DPF * Distortion Factor (DF).


$$\text{Where } DF = \frac{I_{a1,rms}}{I_{a,rms}} = \frac{\left(\frac{\sqrt{6}}{\pi} \right) I_{0,dc}}{\left(\sqrt{\frac{2}{3}} \right) I_{0,dc}} = 0.955$$

$$PF = \frac{P}{S} = \frac{V_{d,avg} \cdot I_{0,dc}}{\sqrt{3} V_{LL} I_{a,rms}} = \frac{V_{d,avg} \cdot I_{0,dc}}{V_{LL,p} \cdot I_{0,dc}} = \frac{V_{d,avg}}{V_{LL,p}} = \frac{-13.545}{400 \cdot \sqrt{2}} = -0.023944$$

$$DPF = PF/DF = -0.024/0.955 = -0.025 \text{ lag or } 0.025 \text{ lead}$$

Therefore the measured DPF is same as with the calculated one.

Case 3: Firing angle of 135 degrees

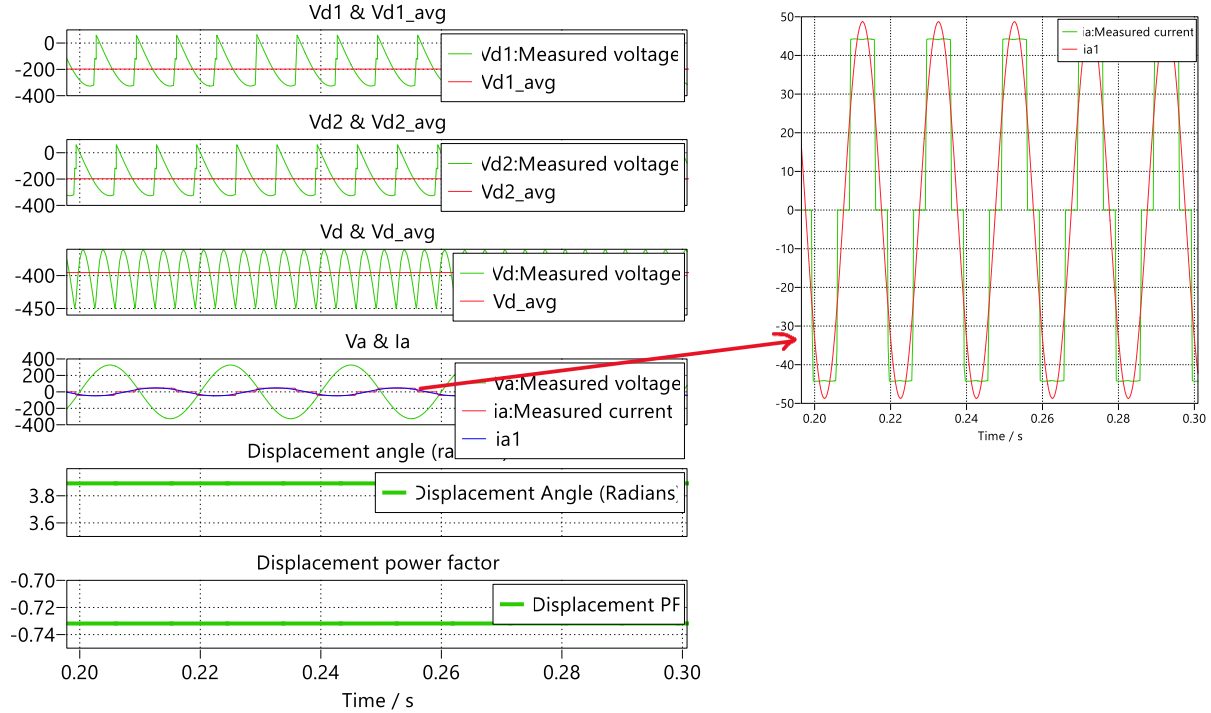

1. Average of Vd1 is -197.693 Volts.
2. Average of Vd2 is -197.693 Volts.
3. Average of Vd is -395.382 Volts.

The average of Vd based on theoretical concept is

$$V_{d_theory} = \left(\frac{3V_{LL,p}}{\pi} \cos \alpha \right) - \left(\frac{3 \cdot 2\pi \cdot 50 \cdot L_s}{\pi} + R \right) I_0 = -381.972 - 13.545 = -395.516 \text{ Volts.}$$

Therefore, the measured output voltage closely matches with the theoretical output voltage.

4. The measured displacement angle (The phase angle of fundamental current of ia with respect to va) is 3.8914 radians or 222.96 (or 137.04) degrees. The measured displacement power factor is 0.731822 lead.

Theoretical Displacement Power Factor (DPF) calculation:

Power Factor (PF) = DPF * Distortion Factor (DF).

$$\text{Where } DF = \frac{I_{a1,rms}}{I_{a,rms}} = \frac{\left(\frac{\sqrt{6}}{\pi} \right) I_{0,dc}}{\left(\sqrt{\frac{2}{3}} \right) I_{0,dc}} = 0.955$$



$$PF = \frac{P}{S} = \frac{V_{d,avg} \cdot I_{0,dc}}{\sqrt{3} V_{LL,p} I_{a,rms}} = \frac{V_{d,avg} \cdot I_{0,dc}}{V_{LL,p} \cdot I_{0,dc}} = \frac{V_{d,avg}}{V_{LL,p}} = \frac{-395.516}{400 \cdot \sqrt{2}} = -0.69918$$

$$DPF = PF/DF = -0.69918/0.955 = -0.732125 \text{ lag or } 0.732125 \text{ lead}$$


Therefore the measured DPF is same as with the calculated one.

Exercise 2: 3-Phase Thyristor Rectifier Bridge (Thyrect3.plecs)


Simulation Model:

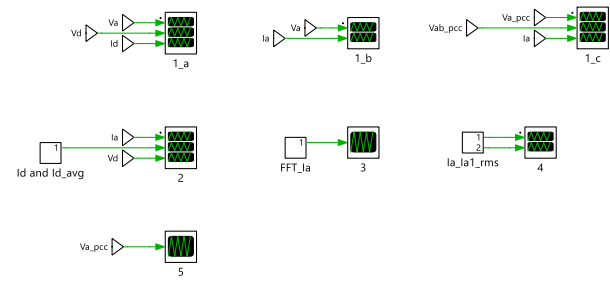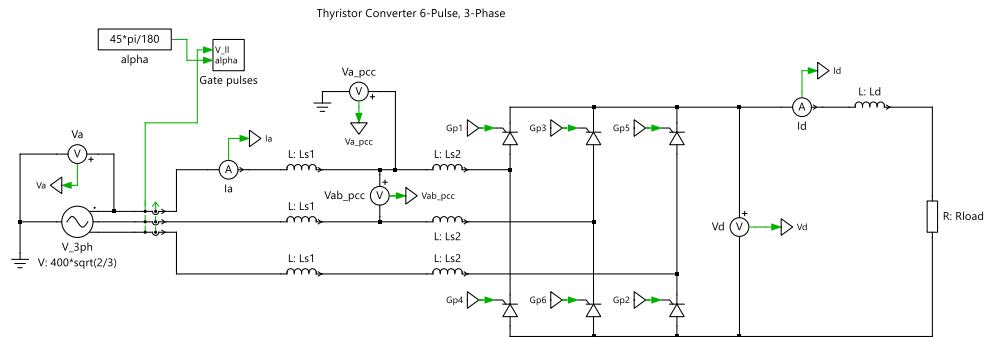

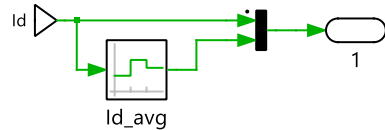
The subsystem of “Id and Id_avg” is as below.



The subsystem of “FFT_Ia” is as below.

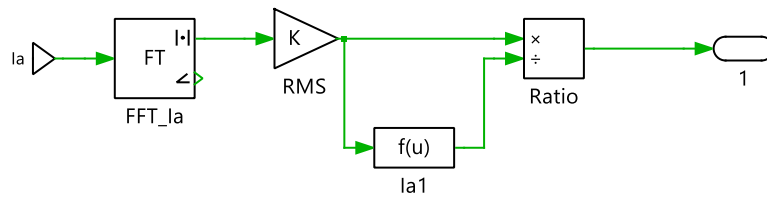


The subsystem of “Ia1_rms” is as below.

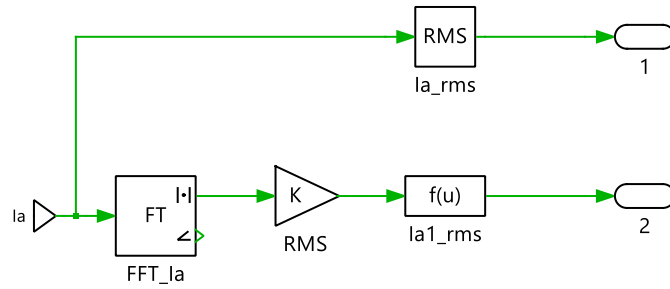


Waveforms:

P1:


Data			
Name	Cursor 1	Cursor 2	Mean
Time	0.92	0.96	
✓ Va	<input checked="" type="checkbox"/>		
✓ 1.36645e-08	<input checked="" type="checkbox"/>	1.26232e-08	2.01575e-09
✓ Vd	<input checked="" type="checkbox"/>		
✓ 295.04	<input checked="" type="checkbox"/>	295.04	367.266
✓ Id	<input checked="" type="checkbox"/>		
✓ 47.0447	<input checked="" type="checkbox"/>	47.0448	45.9082

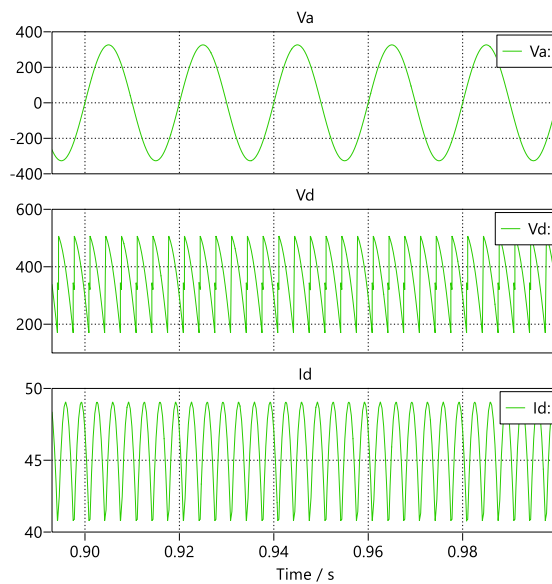

Data			
Name	Cursor 1	Cursor 2	RMS
Time	0.92	0.96	
✓ Va	<input checked="" type="checkbox"/>		
✓ 1.36645e-08	<input checked="" type="checkbox"/>	1.26232e-08	230.94
✓ Ia	<input checked="" type="checkbox"/>		
✓ -47.0447	<input checked="" type="checkbox"/>	-47.0448	37.3753

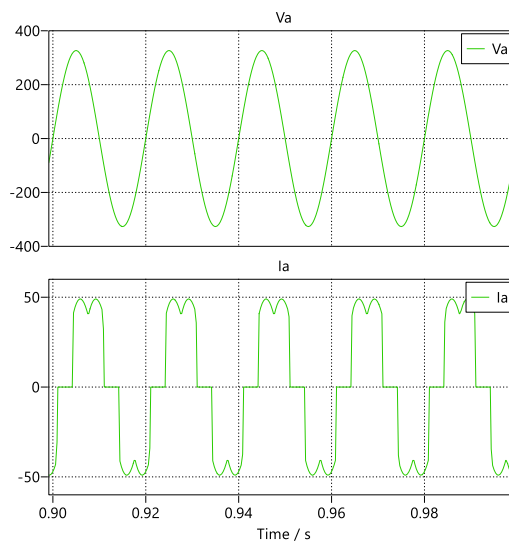

Data			
Name	Cursor 1	Cursor 2	RMS
Time	0.92	0.96	
✓ Va_pcc	<input checked="" type="checkbox"/>		
Va_pcc:	<input checked="" type="checkbox"/> -1.01647	-1.01648	229.408
✓ Vab_pcc	<input checked="" type="checkbox"/>		
Vab_pcc:	<input checked="" type="checkbox"/> 281.826	281.826	397.346
✓ Ia	<input checked="" type="checkbox"/>		
Ia:	<input checked="" type="checkbox"/> -47.0447	-47.0448	37.3753

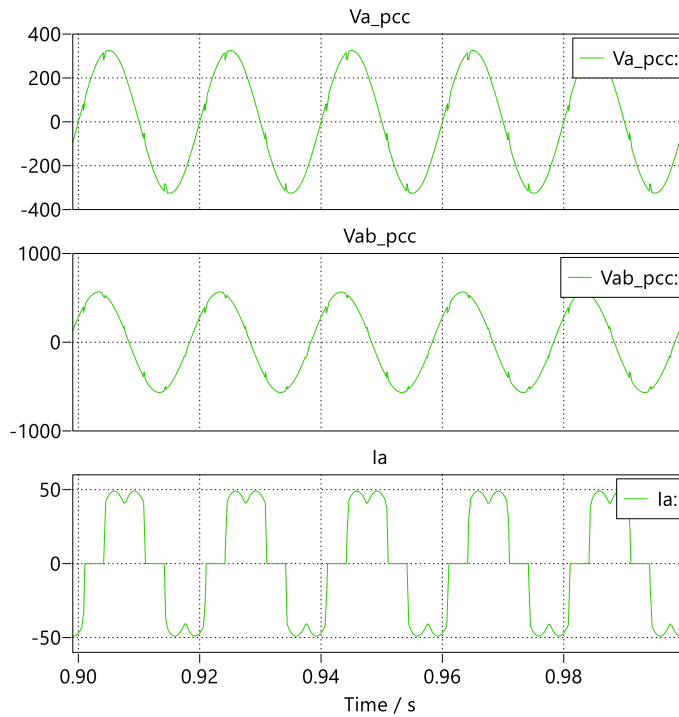

P2:

Commutation interval from the given equation is:

$$\cos(\alpha + u) = \cos \alpha - \frac{2\omega L_s}{\sqrt{2}V_{LL}} I_d$$


$$\cos(45^\circ + u) = \cos 45^\circ - \frac{2 * (2\pi * 50) * (0.2 + 1) * 10^{-3}}{\sqrt{2} * 400} * 45.9082$$

$$\cos\left(\frac{\pi}{4} + u\right) = \cos 45^\circ - 0.06118942755 = 0.64591735364$$


$$\frac{\pi}{4} + u = \cos^{-1} 0.64591735364 = 0.8706$$

$$u = 0.0852018 \text{ radians}$$
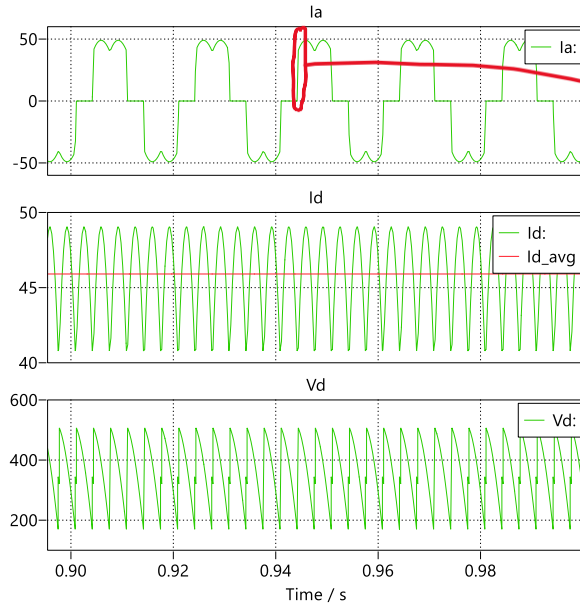
$$u = 0.0852018 * \frac{0.01}{\pi} = 0.2712 \text{ ms}$$



Data				
Name	Cursor 1	Cursor 2	Delta	Mean
Time	0.9	0.98	0.08	
▼ Ia				
Ia:	-47.0446	-47.0449	-0.000278143	-2.75715e-05
▼ Id				
Id:	47.0446	47.0449	0.000278143	45.9082

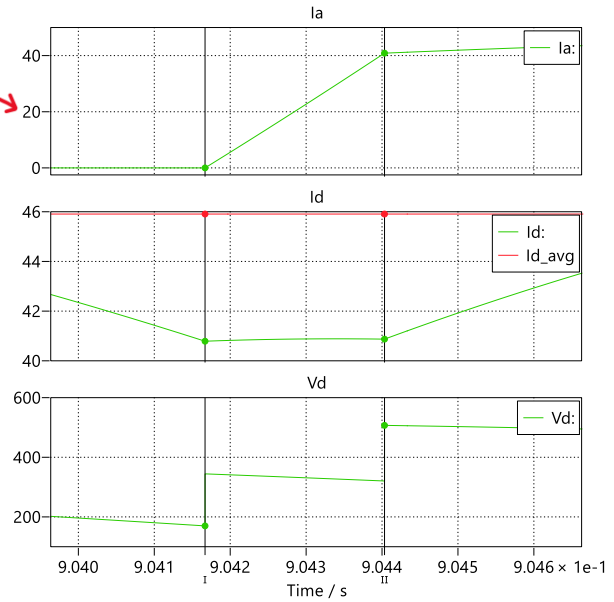

Data				
Name	Cursor 1	Cursor 2	Delta	Mean
Time	0.904167	0.904403	0.000236412	

Id_avg value is 45.9082 A. The commutation interval from the plot is noted as $u = 0.236412$ ms.


There is a considerable difference in u between the calculated and measured ones. This is because of difference in Id magnitude considered. In the measurement plot, commutation period is measured till id reaches 40.873 A whereas in the given equation id is considered as 45.9082.

If we consider Id = 40.873 in the given equation, we get

$$u = 0.0756 \text{ radians}$$


$$u = 0.0756 * \frac{0.01}{\pi} = 0.2406 \text{ ms}$$

P3:

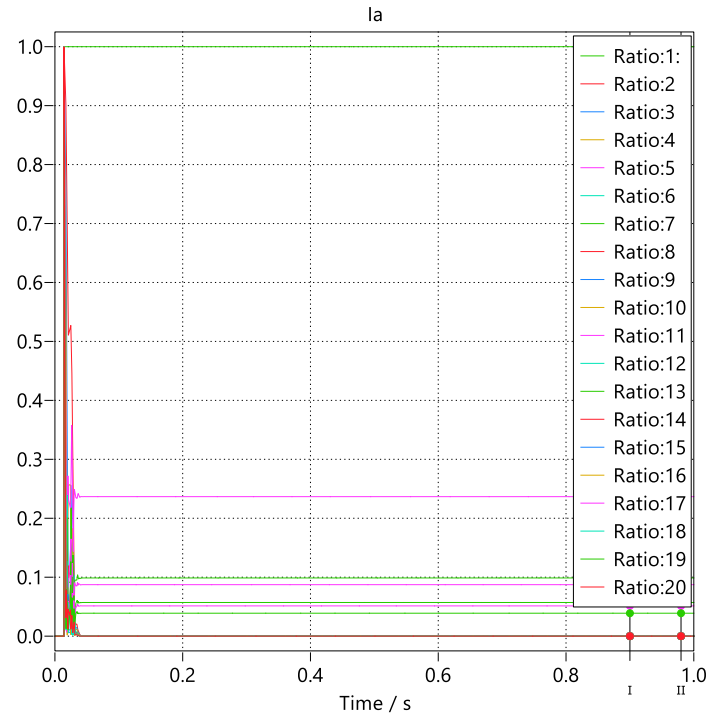

Name		Cursor 1	Cursor 2
Time		0.9	0.98
✓ Ia	<input checked="" type="checkbox"/>		
Ratio:1:		<input checked="" type="checkbox"/> 1	1
Ratio:2:		<input checked="" type="checkbox"/> 2.00141e-07	1.70523e-07
Ratio:3:		<input checked="" type="checkbox"/> 1.00988e-07	8.60541e-08
Ratio:4:		<input checked="" type="checkbox"/> 3.58158e-07	3.05171e-07
Ratio:5:		<input checked="" type="checkbox"/> 0.236646	0.236645
Ratio:6:		<input checked="" type="checkbox"/> 5.98083e-07	5.09593e-07
Ratio:7:		<input checked="" type="checkbox"/> 0.0987365	0.0987372
Ratio:8:		<input checked="" type="checkbox"/> 2.59477e-07	2.21084e-07
Ratio:9:		<input checked="" type="checkbox"/> 1.69327e-07	1.4427e-07
Ratio:10:		<input checked="" type="checkbox"/> 2.77074e-07	2.3608e-07
Ratio:11:		<input checked="" type="checkbox"/> 0.0873471	0.0873471
Ratio:12:		<input checked="" type="checkbox"/> 6.03085e-07	5.13854e-07
Ratio:13:		<input checked="" type="checkbox"/> 0.0571182	0.0571184
Ratio:14:		<input checked="" type="checkbox"/> 2.73835e-07	2.33322e-07
Ratio:15:		<input checked="" type="checkbox"/> 2.10997e-07	1.79777e-07
Ratio:16:		<input checked="" type="checkbox"/> 3.10871e-07	2.64874e-07
Ratio:17:		<input checked="" type="checkbox"/> 0.051338	0.0513379
Ratio:18:		<input checked="" type="checkbox"/> 5.57833e-07	4.75302e-07
Ratio:19:		<input checked="" type="checkbox"/> 0.0389231	0.0389232
Ratio:20:		<input checked="" type="checkbox"/> 2.2683e-07	1.93273e-07

The significant harmonic components are 5, 7, 11, 13, 17 and 19.

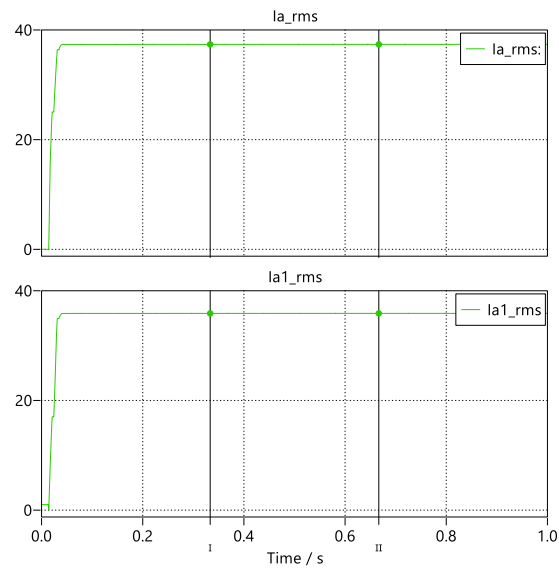P4:

Name		Cursor 1	Cursor 2
la_rms:			37.3703
la1_rms			37.3738
la1_rms			35.8719
			35.8752

Power Factor (PF) = DPF * Distortion Factor (DF).

$$\text{Where DF} = \frac{I_{a1,rms}}{I_{a,rms}} = \frac{35.8752}{37.3738} = 0.96$$


$$\text{PF} = \frac{P}{S} = \frac{V_{d,avg} * I_{0,dc}}{\sqrt{3} V_{LL} I_{a,rms}} = \frac{367.266 * 45.9082}{\sqrt{3} * 400 * 37.3738} = 0.651153$$

The values of $V_{d,avg}$, $I_{0,dc}$ are obtained from figures of P1.

$$\text{DPF} = \text{PF} / \text{DF} = 0.651153 / 0.96 = 0.67828 \text{ lag.}$$

P5:**a. Line-notch depth ρ (%)**

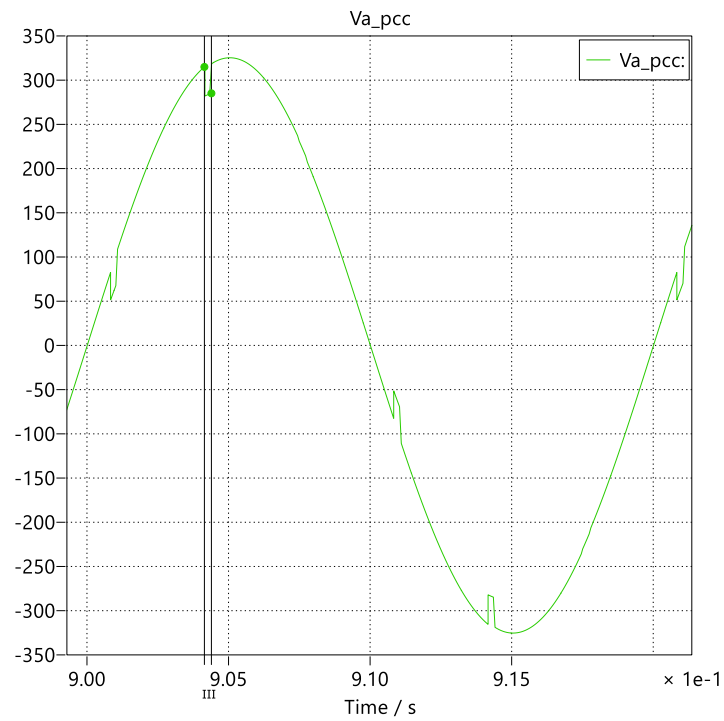It is the ratio of peak-peak deviation from the actual voltage signal to the peak of actual voltage.




Name	Cursor 1	Cursor 2	Delta
Time	0.904148	0.904395	0.000247353
✓ Va_pcc	<input checked="" type="checkbox"/>		
Va_pcc:	<input checked="" type="checkbox"/> 314.959	285.116	-29.8434

Peak to peak deviation is 29.8434 V and the peak of actual voltage is 325.32 V. So,

$$\text{Line notch depth} = \frac{29.8434}{325.32} \times 100 = 9.1735\%$$

b. Line-notch area

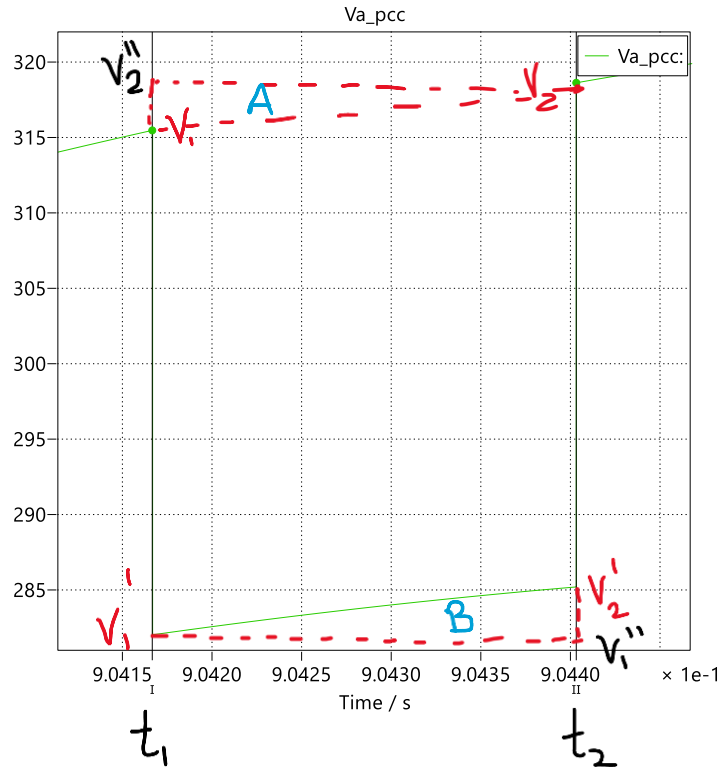

Name	Cursor 1	Cursor 2
Time	0.904167	0.904403
✓ Va_p...	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
~	<input checked="" type="checkbox"/> 315.47	318.626

Line-notch area = Area of rectangle $V_1'V_1''V_2V_2''$
 $= (V_2 - V_1'') * (t_2 - t_1)$
 $= (318.626 - 282.027) * (0.904403 - 0.904167)$
 $= 0.008637364 \text{ voltsec}$

P6:

The average value of V_d from the figures of P1 is 367.266 V.

The given equation for average of V_d is


$$V_d = 1.35V_{LL} \cos \alpha - \frac{3\omega L_s}{\pi} I_d$$

Substituting $V_{LL} = 400$, $\alpha = 45^\circ$, $\omega = 2\pi * 50$, $L_s = L_{s1} + L_{s2} = 1.2e^{-3}$, $I_d = 45.9082$ (from P1 figures), we get $V_{d_{avg}} = 365.31 \text{ V}$.


The calculated value matches close to the measured value.

Exercise 3: Three-Phase, PWM Inverter (PWINV3.plecs)


Simulation Model:

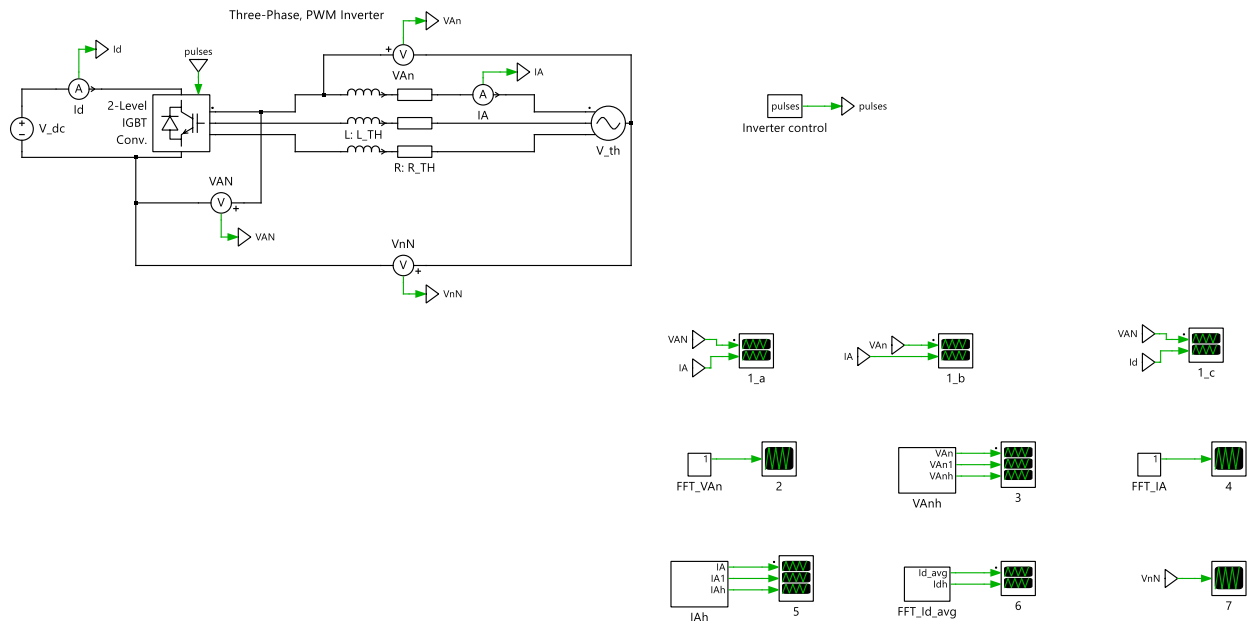

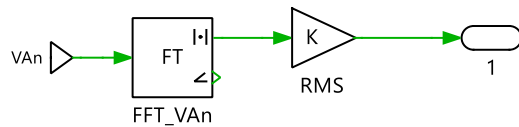
The subsystem of “FFT_VAn” is as below. The similar model is used in “FFT_IA” subsystem except the input which is I_A instead of V_{An} .



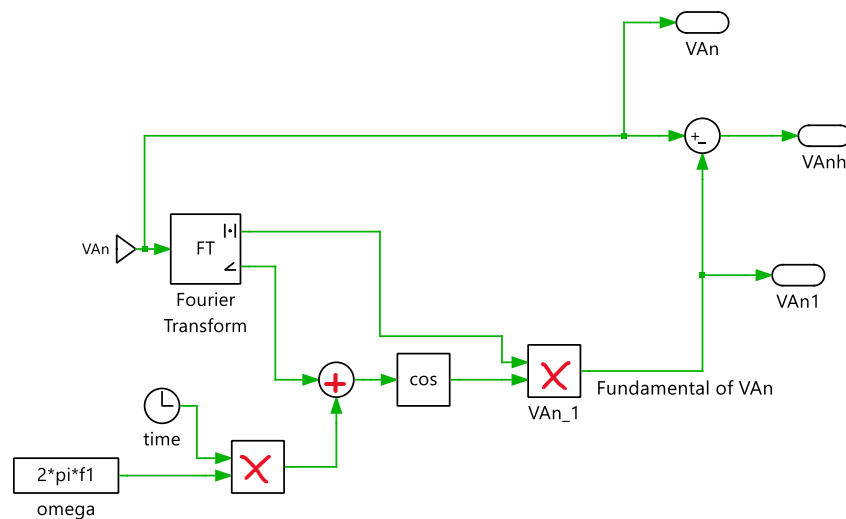The subsystem of “VAnh” is as below. The similar model is used in “IAh” subsystem except the input which is I_A instead of V_{An} .




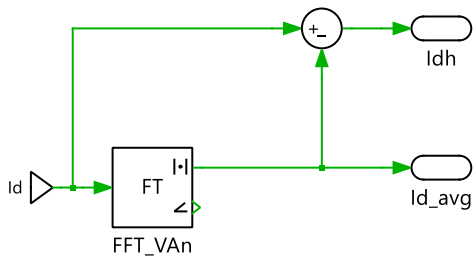The subsystem of “FFT_Id_avg” is as below.




Waveforms:


P1:

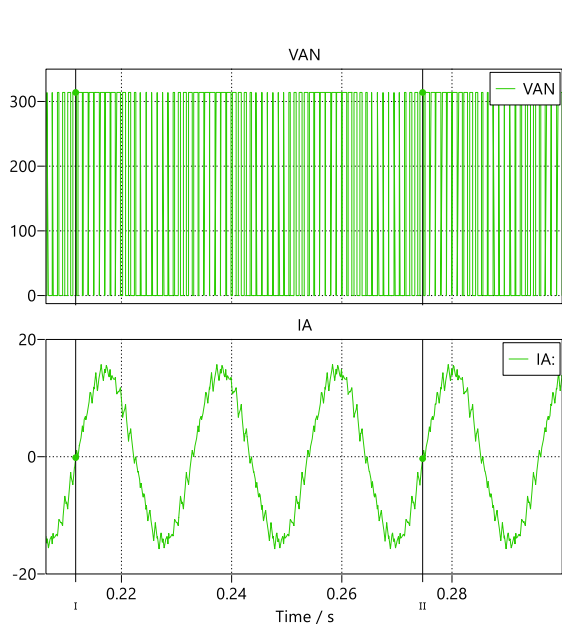

Name	Cursor 1	Cursor 2	RMS
Time	0.211693	0.274673	
✓ VAN	<input checked="" type="checkbox"/>		
✓ 313.97	<input checked="" type="checkbox"/>	313.97	221.975
✓ IA	<input checked="" type="checkbox"/>		
✓ -0.156453	<input checked="" type="checkbox"/>	-0.326257	10.3125

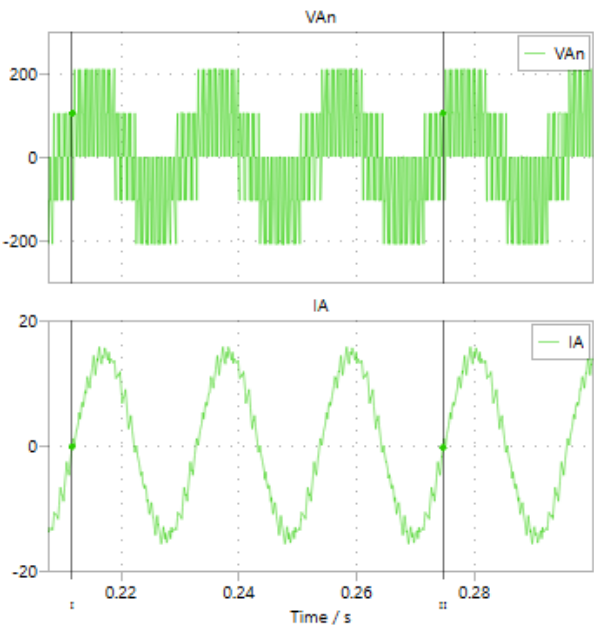


Name	Cursor 1	Cursor 2	RMS
Time	0.211693	0.274673	
✓ VAn	<input checked="" type="checkbox"/>		
✓ 104.657	<input checked="" type="checkbox"/>	104.657	131.257
✓ IAn	<input checked="" type="checkbox"/>		
✓ -0.15785	<input checked="" type="checkbox"/>	-0.327673	10.3125

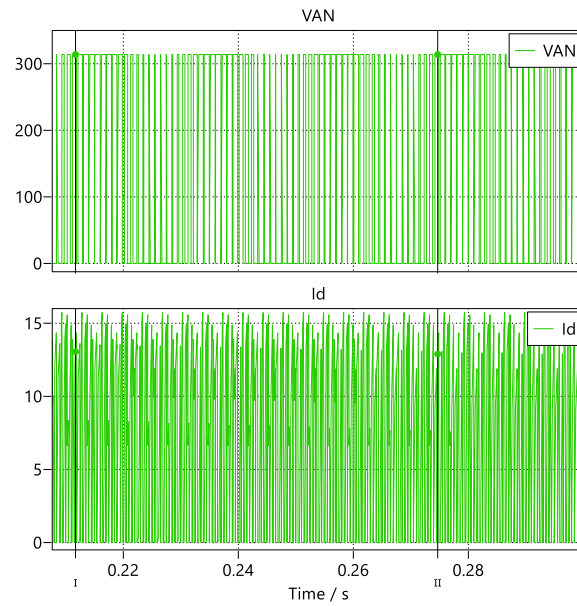

Name	Cursor 1	Cursor 2	Mean	RMS
Time	0.211693	0.274673		
✓ VAN	<input checked="" type="checkbox"/>			
VAN	<input checked="" type="checkbox"/> 313.97	313.97	156.935	221.975
✓ Id	<input checked="" type="checkbox"/>			
Id	<input checked="" type="checkbox"/> 13.055	12.8883	9.14061	10.6975


P2:

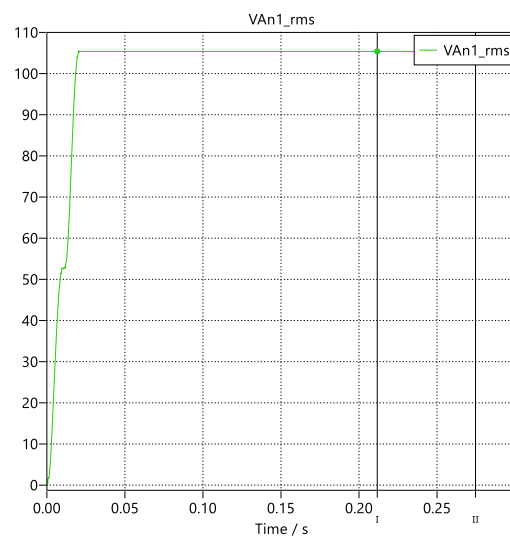

Name	Cursor 1	Cursor 2	RMS
Time	0.211693	0.274673	
✓ VAn1_rms	<input checked="" type="checkbox"/>		
VAn1_rms	<input checked="" type="checkbox"/> 105.388	105.388	105.388


The measured fundamental voltage V_{An1}^{rms} ($f_1 = 47.619 \text{ Hz}$) is same as the calculated i.e., 105.39 V.

P3:

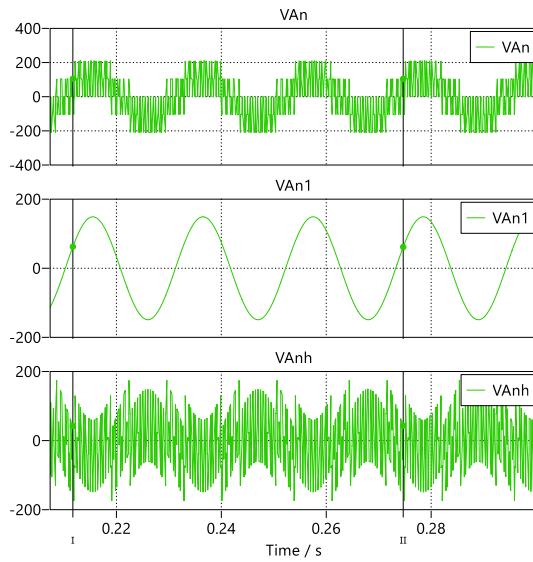

Name	Cursor 1	Cursor 2	RMS
Time	0.211693	0.274673	
✓ VAn	<input checked="" type="checkbox"/>		
VAn	<input checked="" type="checkbox"/> 104.657	104.657	131.257
✓ VAn1	<input checked="" type="checkbox"/>		
VAn1	<input checked="" type="checkbox"/> 62.3589	61.5452	105.399
✓ VAnh	<input checked="" type="checkbox"/>		
VAnh	<input checked="" type="checkbox"/> 42.2978	43.1115	78.237


P4:

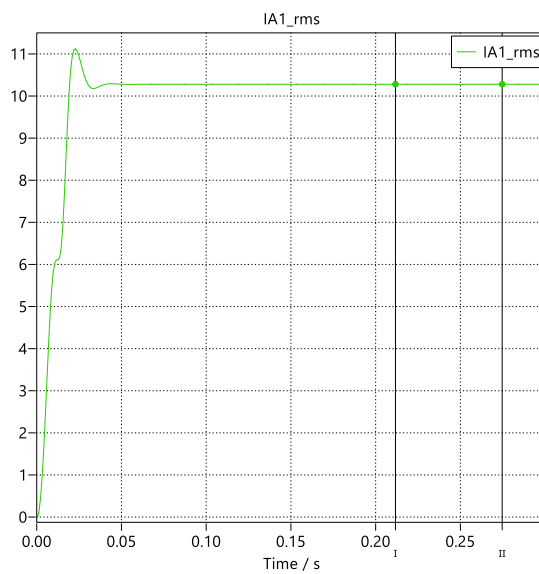

Name	Cursor 1	Cursor 2	RMS
Time	0.211693	0.274673	
✓ IA1_rms	<input checked="" type="checkbox"/>		
IA1_rms	<input checked="" type="checkbox"/> 10.2793	10.2793	10.2793


The measured fundamental current I_{A1}^{rms} ($f_1 = 47.619 \text{ Hz}$) is same as the calculated i.e., 10 A.

P5:

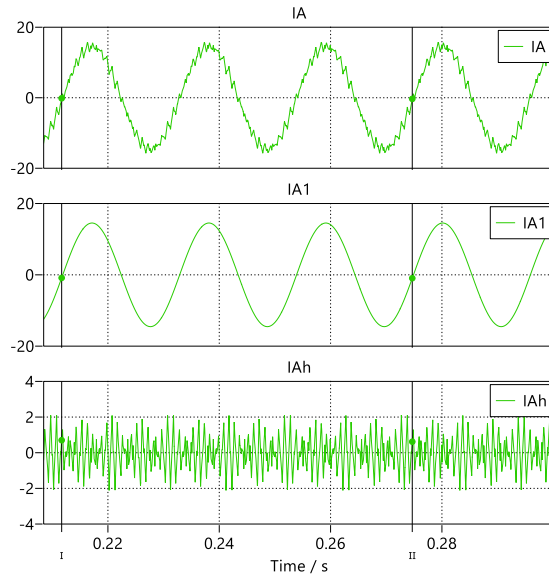

Name	Cursor 1	Cursor 2	RMS
Time	0.211693	0.274673	
✓ IA	<input checked="" type="checkbox"/>		
IA	<input checked="" type="checkbox"/> -0.15785	<input checked="" type="checkbox"/> -0.327673	10.3125
✓ IA1	<input checked="" type="checkbox"/>		
IA1	<input checked="" type="checkbox"/> -0.858458	<input checked="" type="checkbox"/> -0.945553	10.2809
✓ IAh	<input checked="" type="checkbox"/>		
IAh	<input checked="" type="checkbox"/> 0.700608	<input checked="" type="checkbox"/> 0.61788	0.806461

P6:

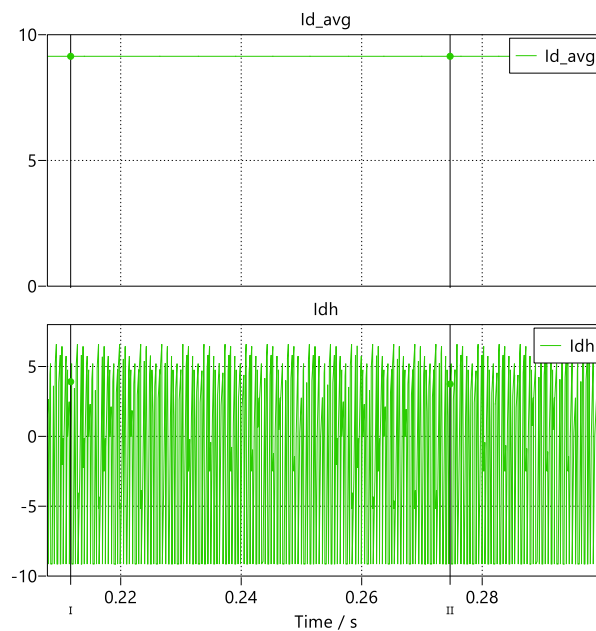

Name	Cursor 1	Cursor 2	Mean	RMS
Time	0.211693	0.274673		
✓ Id_avg	<input checked="" type="checkbox"/>			
Id_avg	<input checked="" type="checkbox"/> 9.14184	<input checked="" type="checkbox"/> 9.14184	9.14184	9.14184
✓ Idh	<input checked="" type="checkbox"/>			
Idh	<input checked="" type="checkbox"/> 3.91317	<input checked="" type="checkbox"/> 3.74648	-0.001233	5.55742


The average value is 9.14184 A and the ripple value is 5.55742 A.

P7:

The mid-point of the DC input voltage is assumed as its reference point N.


Name	Cursor 1	Cursor 2	RMS
Time	0.211693	0.225914	
✓ VnN	<input checked="" type="checkbox"/>		
VnN	<input checked="" type="checkbox"/> 209.313	<input checked="" type="checkbox"/> 1.47438e-13	179.112

VnN is nothing but common mode voltage of the converter.

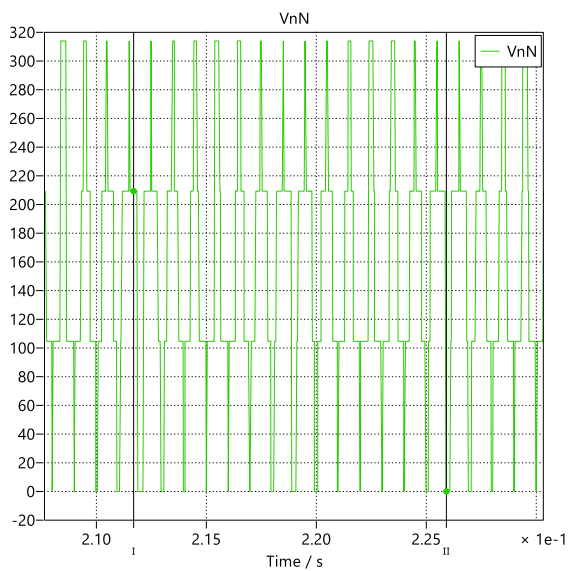


Exercise 4: Three-Phase, Square-Wave Inverter (SQINV3.plecs)


Simulation Model:

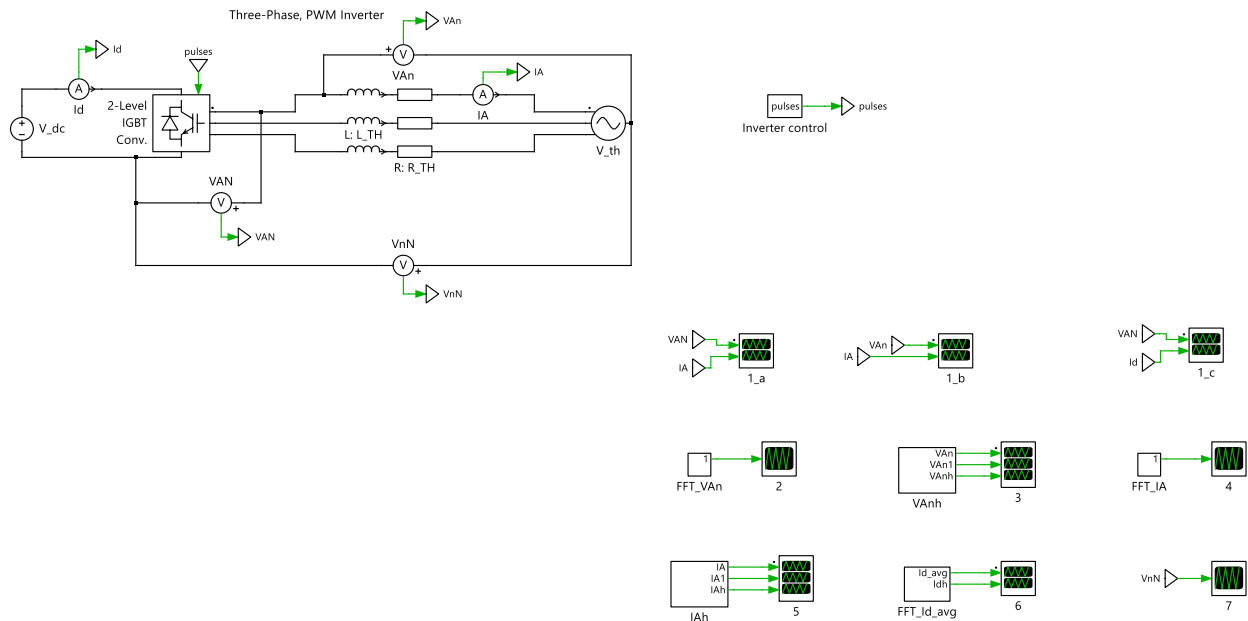

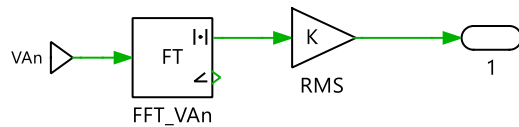
The subsystem of “FFT_VAn” is as below. The similar model is used in “FFT_IA” subsystem except the input which is I_A instead of V_{An} .



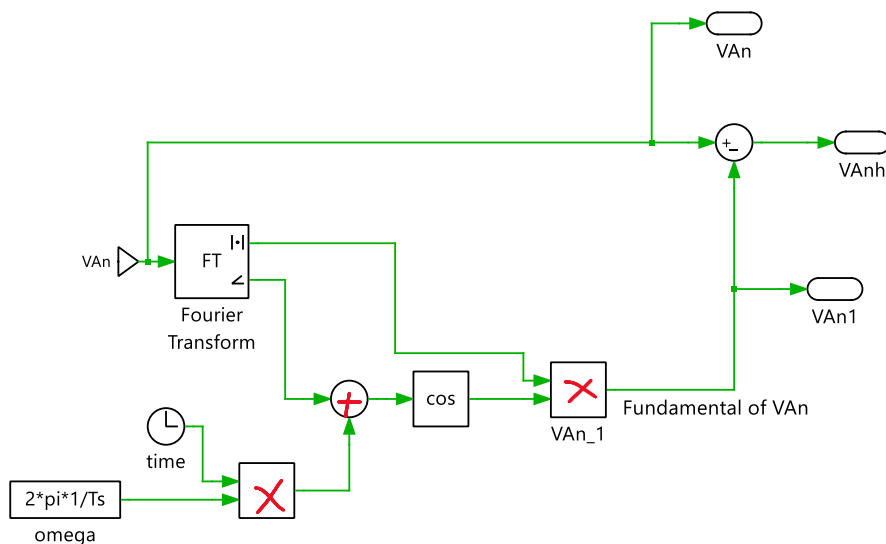The subsystem of “VAnh” is as below. The similar model is used in “IAh” subsystem except the input which is I_A instead of V_{An} .



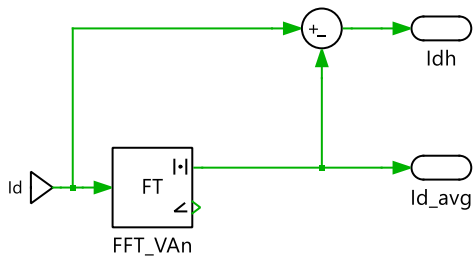
The subsystem of “FFT_Id_avg” is as below.




Fundamental frequency considered in all the applicable PLECS elements is $\frac{1}{T_s=21e-3}$

Waveforms:


P1:

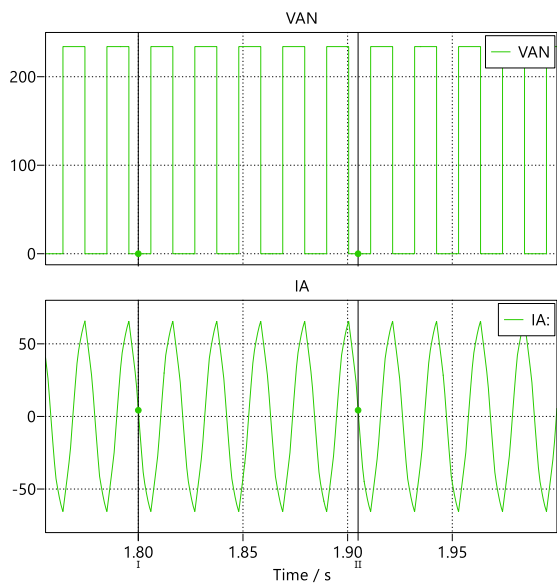

Name	Cursor 1	Cursor 2	RMS
Time	1.8	1.905	
▼ VAN	<input checked="" type="checkbox"/>		
<input checked="" type="checkbox"/> 0	0	0	165.484
▼ IA	<input checked="" type="checkbox"/>		
<input checked="" type="checkbox"/> 4.25193	4.25193	4.25265	43.5731

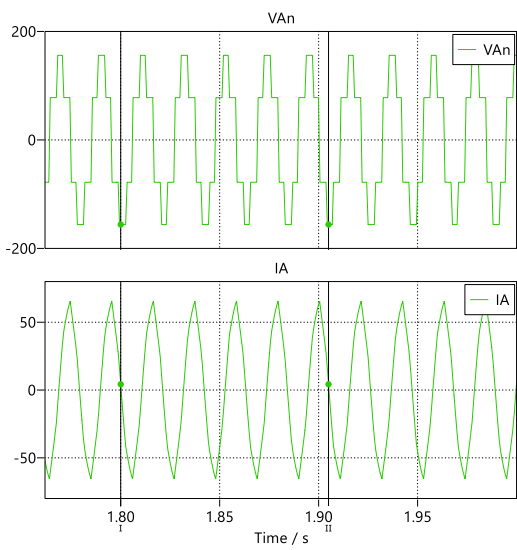


Name	Cursor 1	Cursor 2	RMS
Time	1.8	1.905	
▼ VAn	<input checked="" type="checkbox"/>		
<input checked="" type="checkbox"/> -156.02	-156.02	-156.02	110.323
▼ IA	<input checked="" type="checkbox"/>		
<input checked="" type="checkbox"/> 4.25193	4.25193	4.25265	43.5731

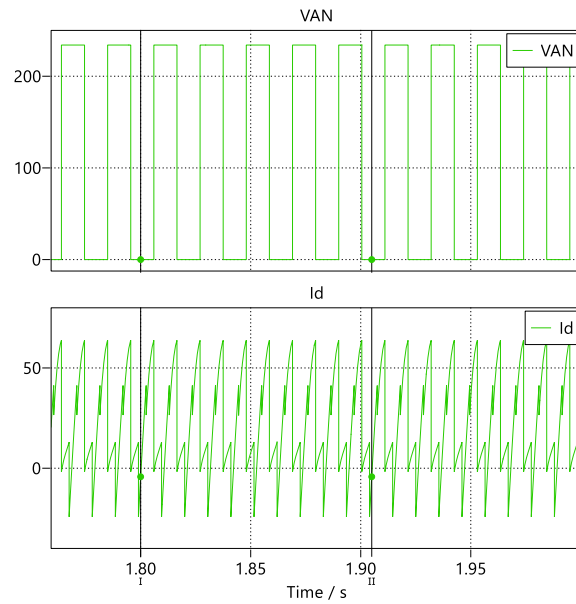

Name	Cursor 1	Cursor 2	Mean	RMS
Time	1.8	1.905		
✓ VAN	<input checked="" type="checkbox"/>			
VAN ~	<input checked="" type="checkbox"/> 0	<input checked="" type="checkbox"/> 0	117.015	165.484
✓ Id	<input checked="" type="checkbox"/>			
Id ~	<input checked="" type="checkbox"/> -4.25193	<input checked="" type="checkbox"/> -4.25265	22.0366	32.3119

P2:

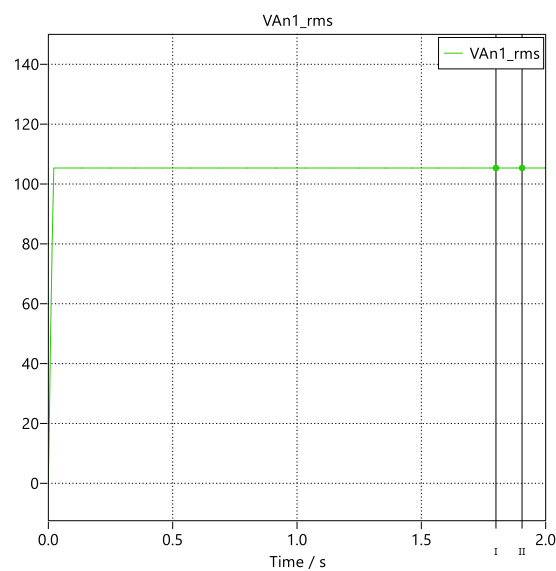


Name	Cursor 1	Cursor 2	RMS
Time	1.8	1.905	
✓ VAn1_rms	<input checked="" type="checkbox"/>		
VAn1_rms ~	<input checked="" type="checkbox"/> 105.351	<input checked="" type="checkbox"/> 105.351	105.351

The measured fundamental voltage V_{An1}^{rms} ($f_1 = 47.619 \text{ Hz}$) is same as the calculated i.e.,


$$V_{LL1}^{rms} = 182.54 \text{ V} \rightarrow V_{An1}^{rms} = \frac{V_{LL1}^{rms}}{\sqrt{3}} = 105.389 \text{ V}.$$

P3:

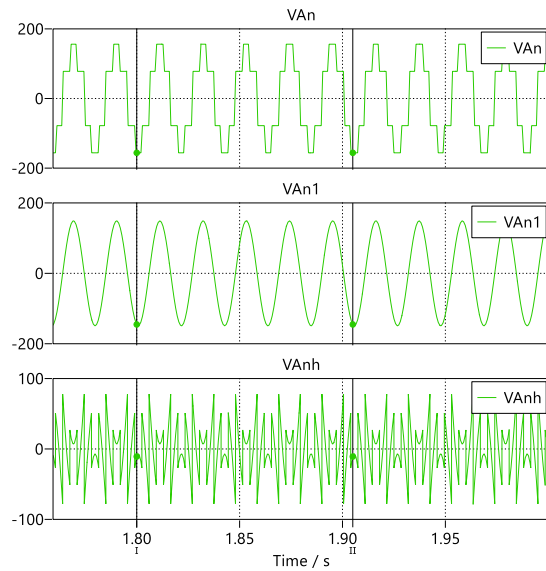

Name		Cursor 1	Cursor 2	RMS
Time		1.8	1.905	
✓ VAn	<input checked="" type="checkbox"/>			
VAn	~	-156.02	-156.02	110.323
✓ VAn1	<input checked="" type="checkbox"/>			
VAn1	~	-145.253	-145.253	105.35
✓ VAnh	<input checked="" type="checkbox"/>			
VAnh	~	-10.7673	-10.7673	32.7474


P4:

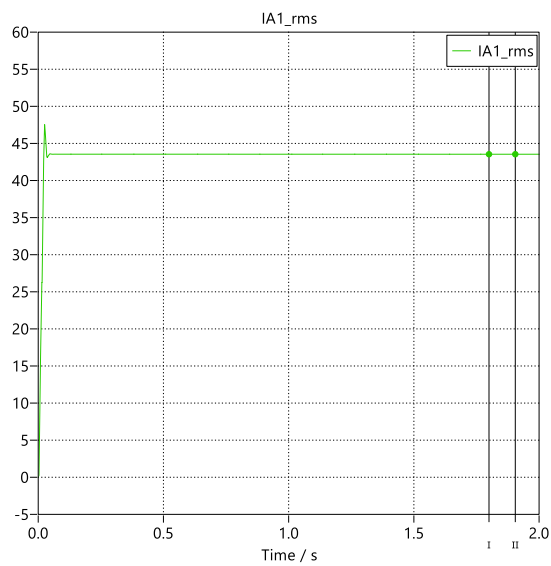

Name		Cursor 1	Cursor 2	RMS
Time		1.8	1.905	
✓ IA1_rms	<input checked="" type="checkbox"/>			
IA1_rms	~	43.5432	43.5428	43.543


The measured fundamental current I_{A1}^{rms} ($f_1 = 47.619 \text{ Hz}$) is not same as the calculated i.e., 10 A. This is due to mismatch in the common mode voltages (CMVs) as we used different PWM schemes. The fundamental RMS CMV in this example is 123.345 V which is less compared to in the previous example (179.059 V). These values could be noted from the figure of P7.

P5:

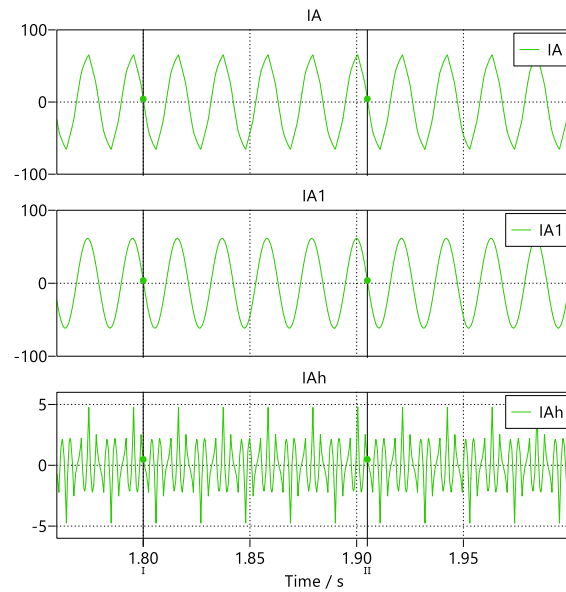

Name	Cursor 1	Cursor 2	RMS
Time	1.8	1.905	
IA	<input checked="" type="checkbox"/>		
IA	<input checked="" type="checkbox"/> 4.25193	4.25265	43.5731
IA1	<input checked="" type="checkbox"/>		
IA1	<input checked="" type="checkbox"/> 3.76824	3.76896	43.5429
IAh	<input checked="" type="checkbox"/>		
IAh	<input checked="" type="checkbox"/> 0.483693	0.483693	1.62081

P6:

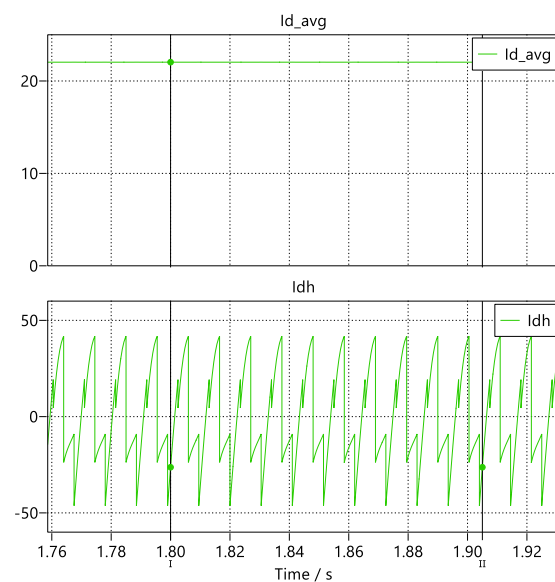

Name	Cursor 1	Cursor 2	Mean	RMS
Time	1.8	1.905		
Id_avg	<input checked="" type="checkbox"/>			
Id_avg	<input checked="" type="checkbox"/> 22.0366	22.0366	22.0366	22.0366
Idh	<input checked="" type="checkbox"/>			
Idh	<input checked="" type="checkbox"/> -26.2886	-26.2893	-7.5835e-06	23.6315


The average value is 22.0366 A and the ripple value is 23.6315 A.

P7:

The mid-point of the DC input voltage is assumed as its reference point N.


Name	Cursor 1	Cursor 2	RMS
Time	1.8	1.905	
VnN	<input checked="" type="checkbox"/>		
VnN	<input checked="" type="checkbox"/> 156.02	156.02	123.345

VnN is nothing but common mode voltage of the converter.

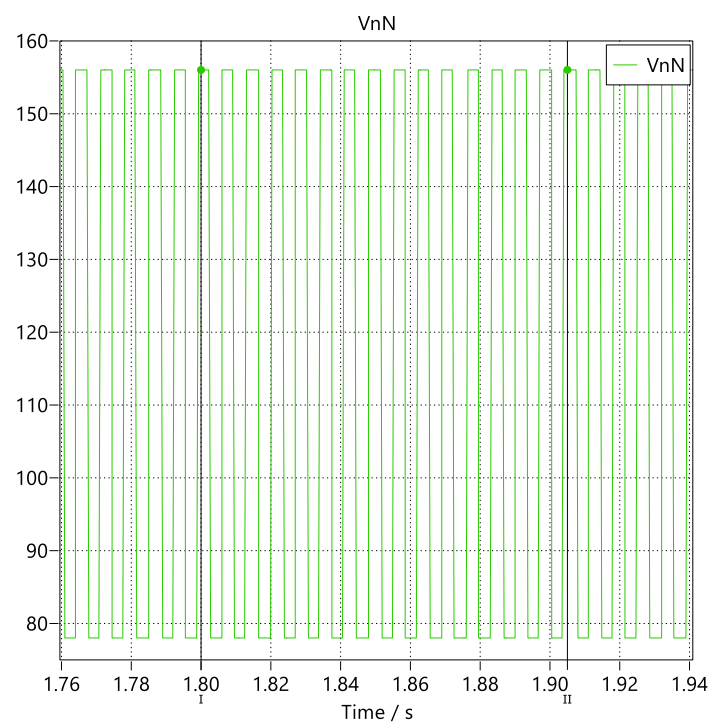


Exercise 5: Three-Phase, PWM Inverter with a Three-Phase Rectifier Input (PWMInv3_Rect.plecs)


Simulation Model:

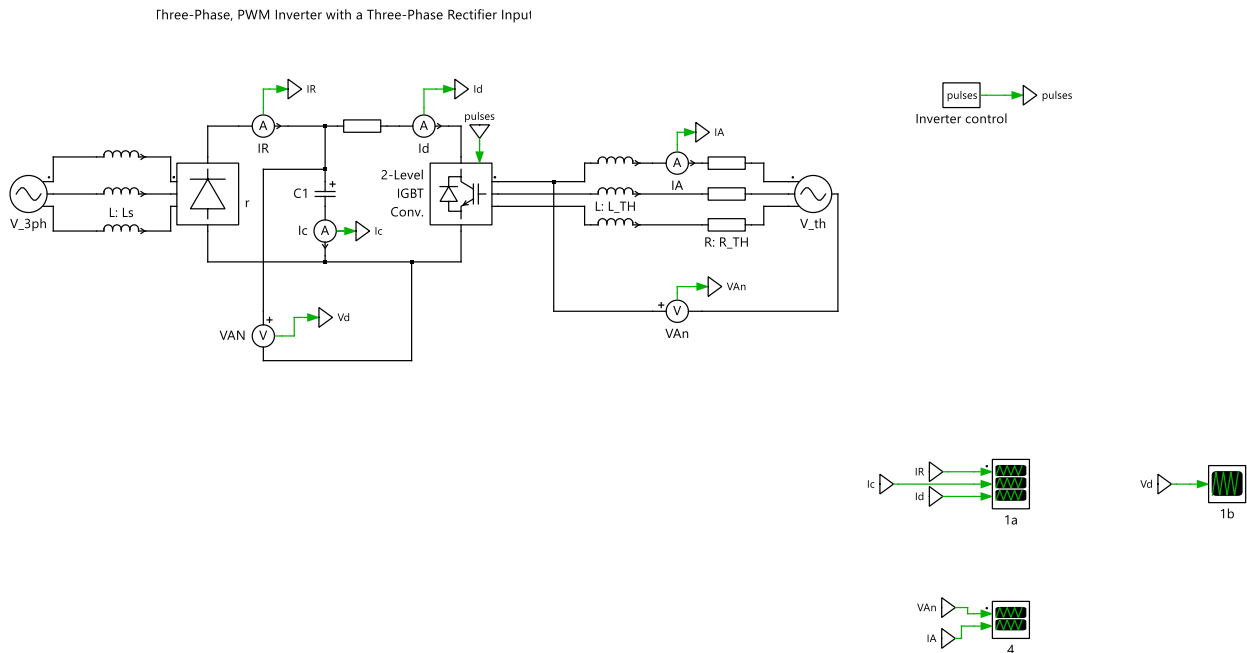

Waveforms:

P1:

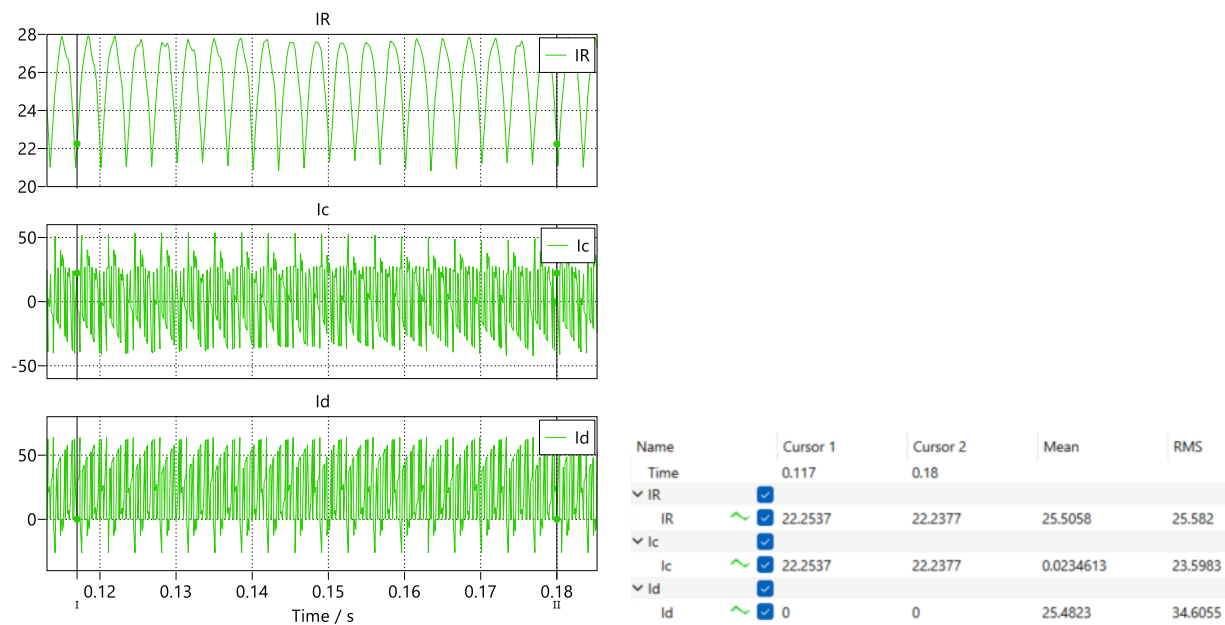


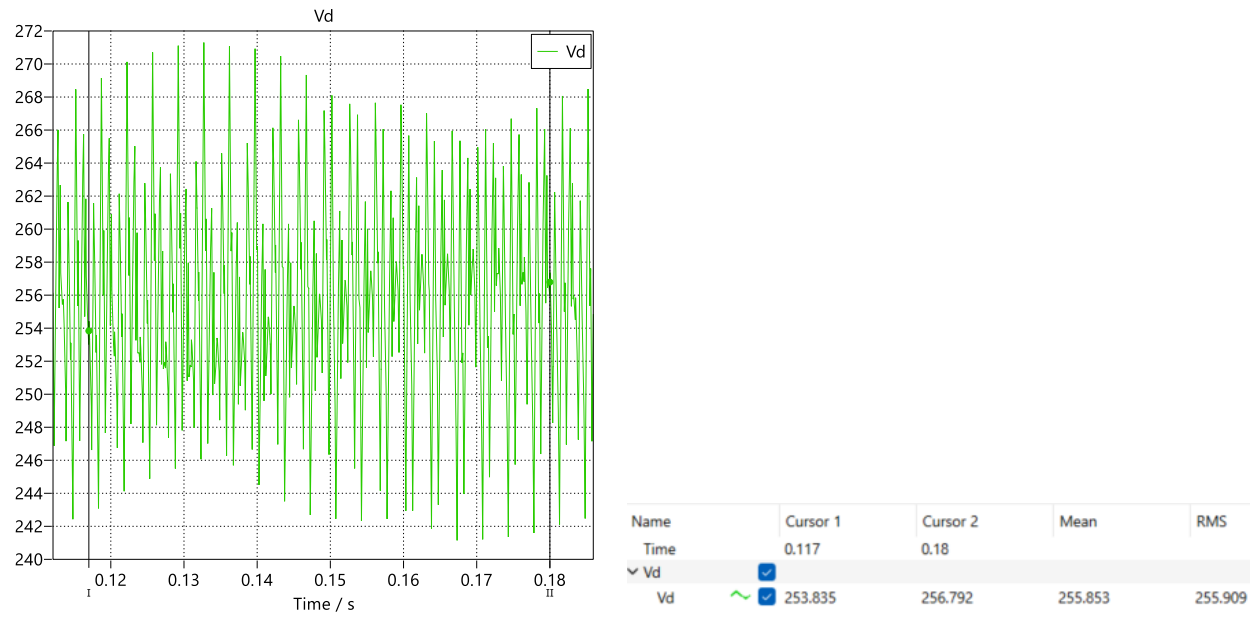

P2:

From the above figures, the RMS values of currents (i_R , i_c & i_d) are 25.582 A, 23.5983 A, and 34.6055 A respectively.


P3:

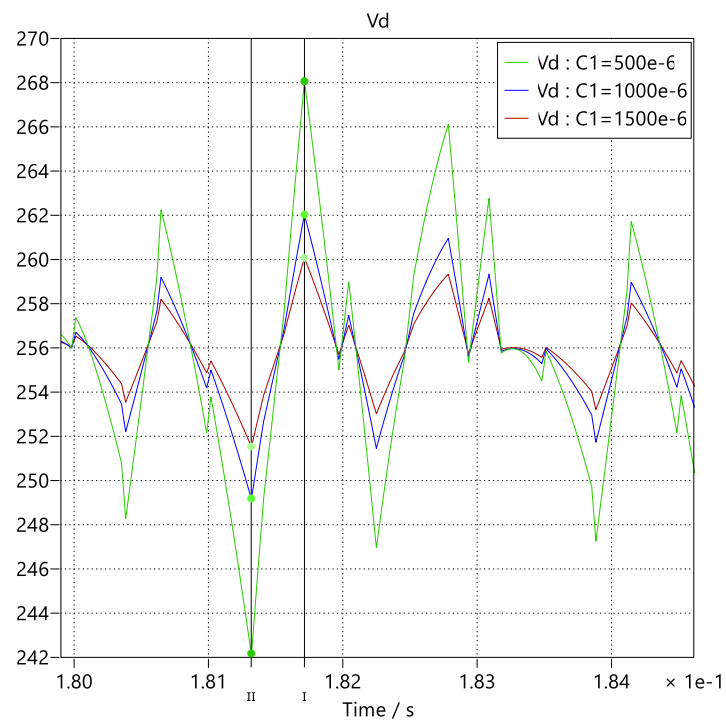

Name	Cursor 1	Cursor 2	Delta	Mean	RMS
Time	0.18132	0.181715	0.000394573		
✓ Vd					
Vd	242.109	268.064	25.9548	255.29	255.392
Vd	249.157	262.033	12.8764	255.698	255.723
Vd	251.516	260.077	8.5615	255.865	255.877

The RMS and Average values of DC-link voltage are same for all capacitance values but the peak-peak voltage is inversely proportional to the capacitance value.

P4:

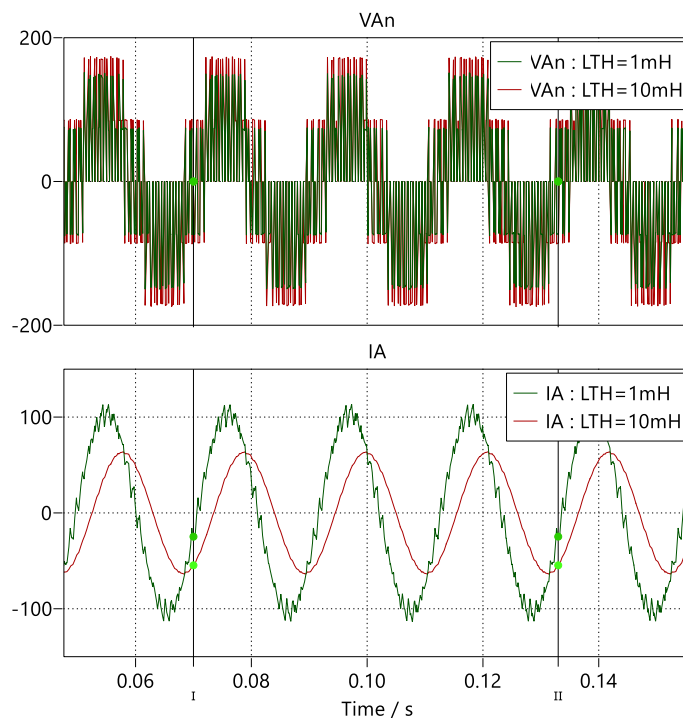


Name	Cursor 1	Cursor 2	Mean	RMS
Time	0.07	0.133		
✓ VAn				
VAn	-7.10543e-15	7.10543e-15	0.00740513	91.7983
VAn	-7.10543e-15	7.10543e-15	-0.017328	107.027
✓ IA				
IA	-24.7867	-24.7572	0.00347102	73.6417
IA	-54.6829	-54.6964	-0.0075881	44.6689


As the filter inductance increases, the current quality is improved.

Exercise 6: 3-Phase, Switch-Mode Interconnection for a Bi-directional-Power-Flow (3Ph_Conn.plecs)


Simulation Model:

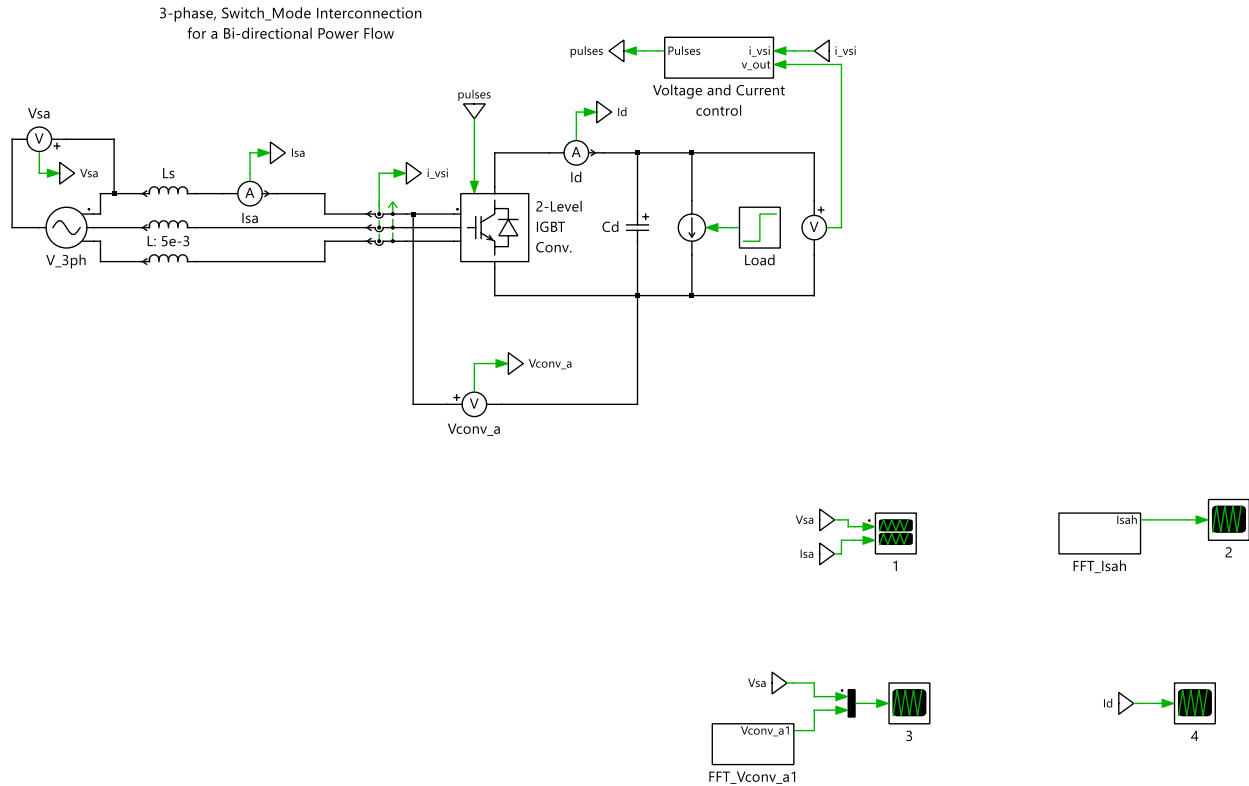

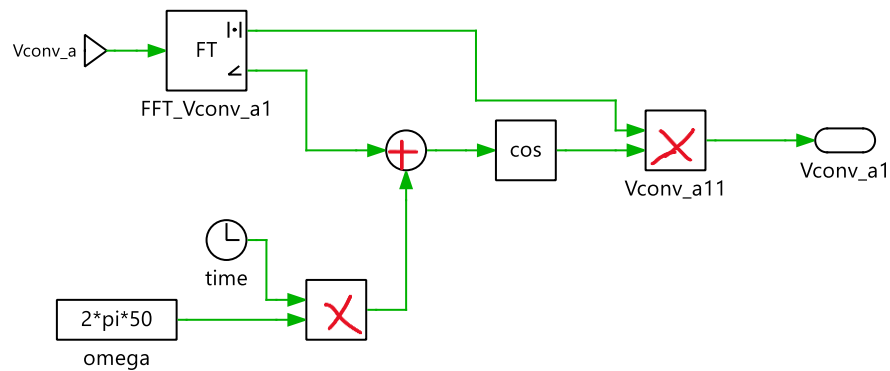The subsystem of “FFT_Vconv_a1” is as below.




The subsystem of “FFT_Isah” is as below.

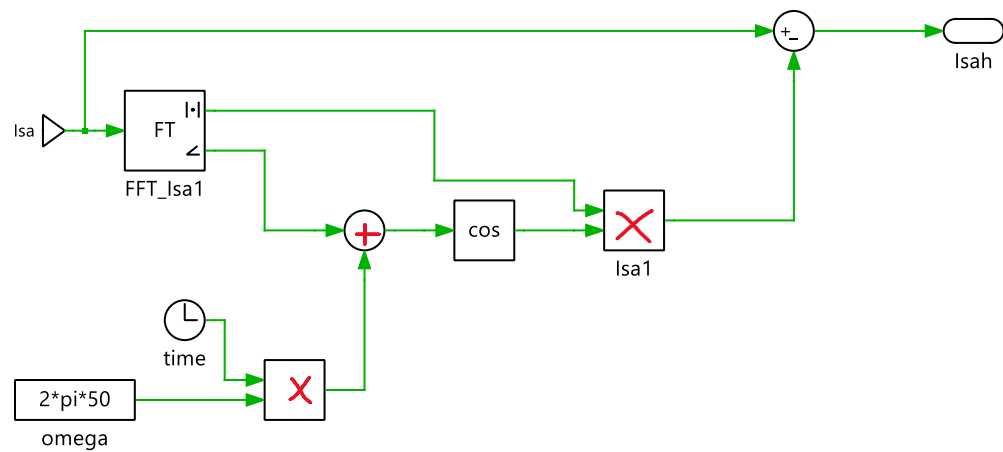


Waveforms:

P1:

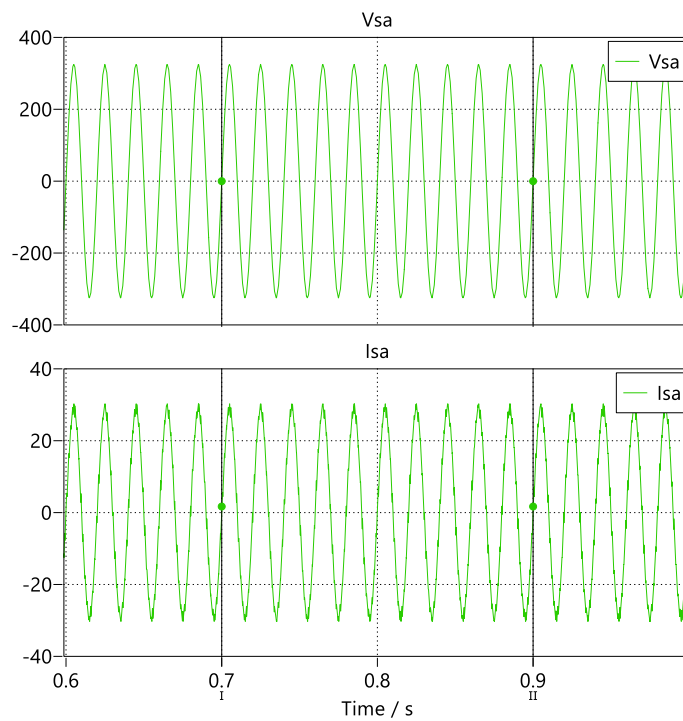


Name	Cursor 1	Cursor 2	RMS
Time	0.7	0.9	
✓ Vsa	✓	✓	
✓	-7.15872e-12	-1.27269e-12	229.785
✓ Isa	✓	✓	
✓	1.69184	1.69184	20.3213

P2:

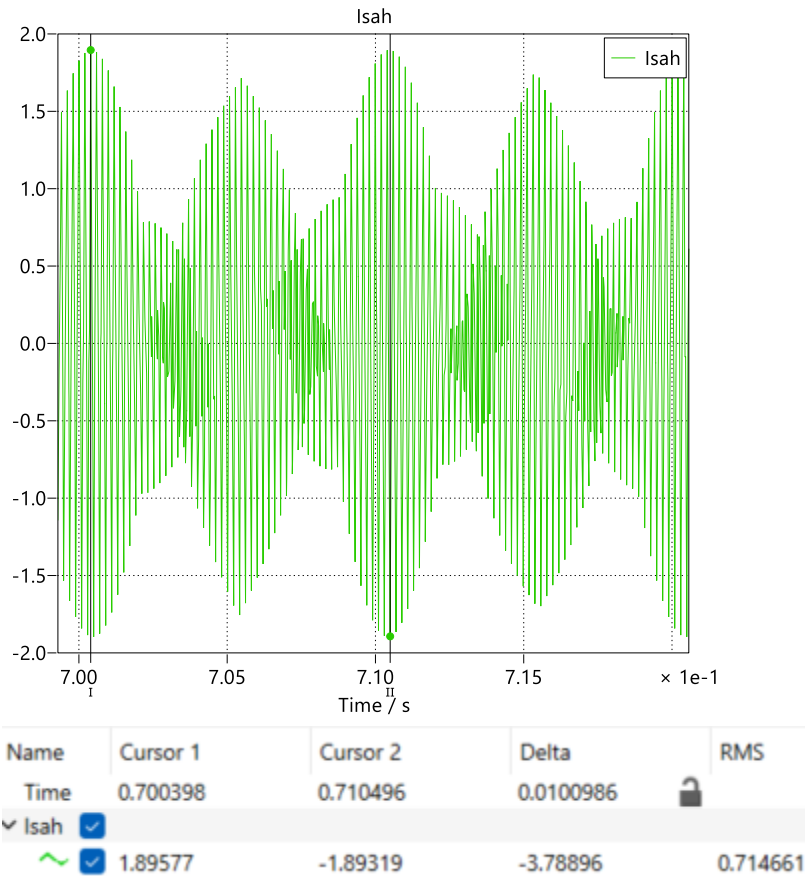


So peak-peak ripple current is 3.78896 A.

P3:

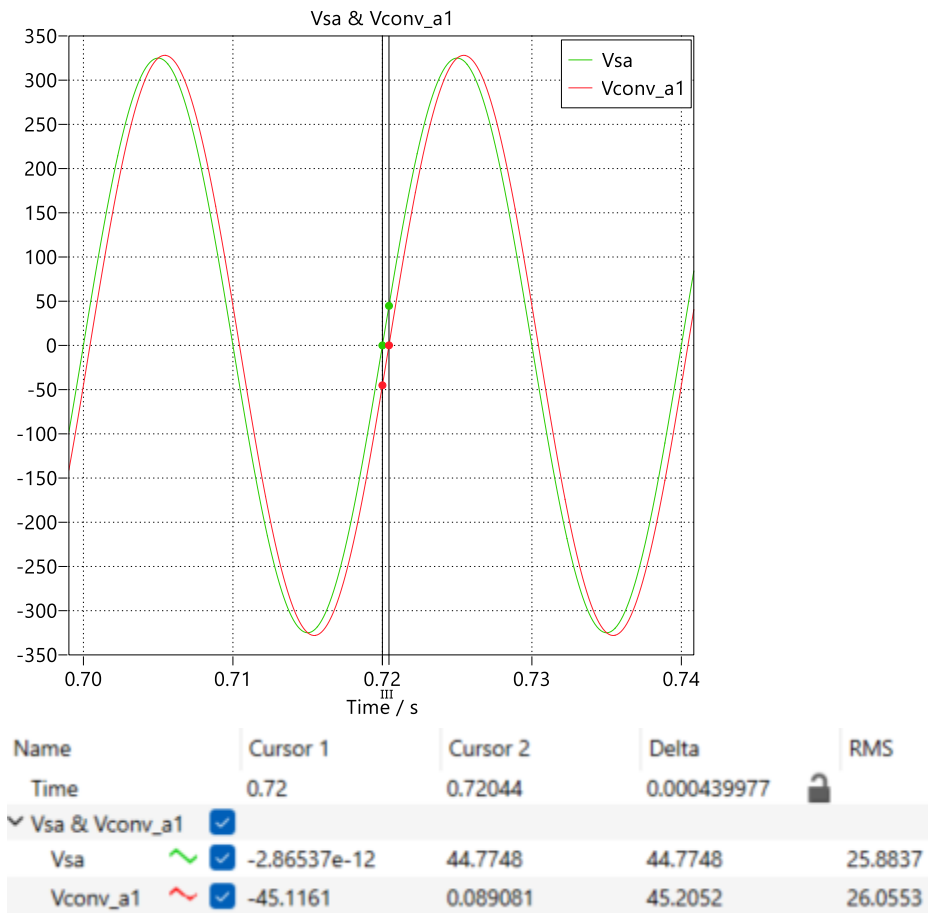

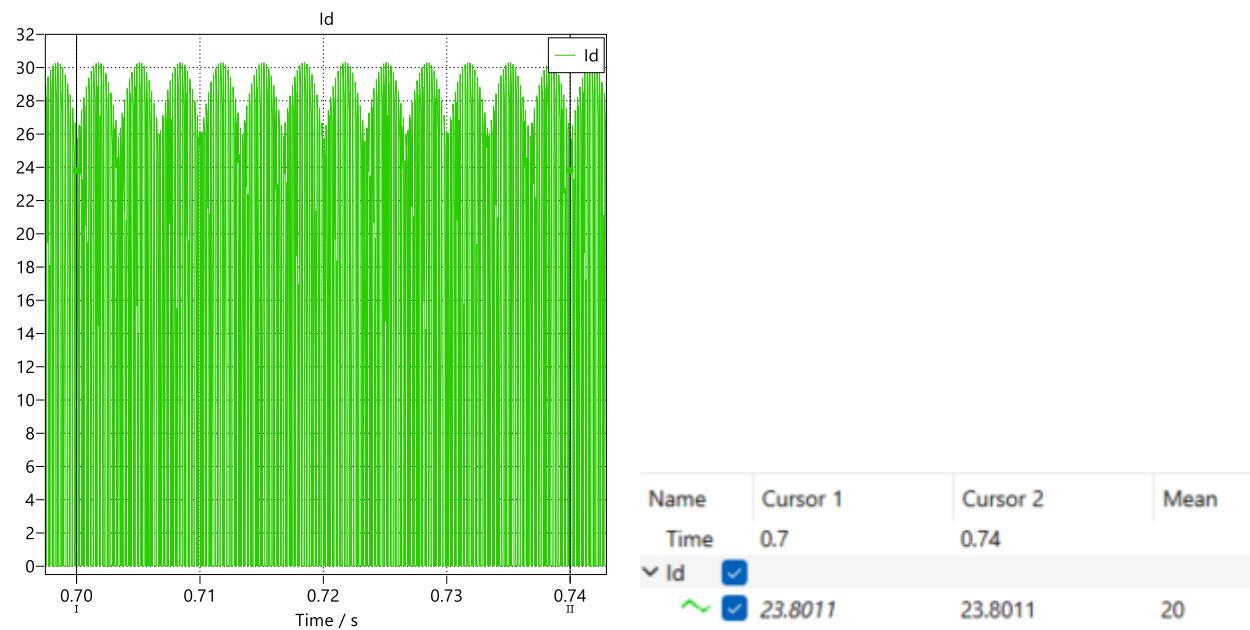
Vconv1 lags Vs by a time of 0.439977 ms and its equivalent angle in degrees is 7.919586.



P4:



P5:

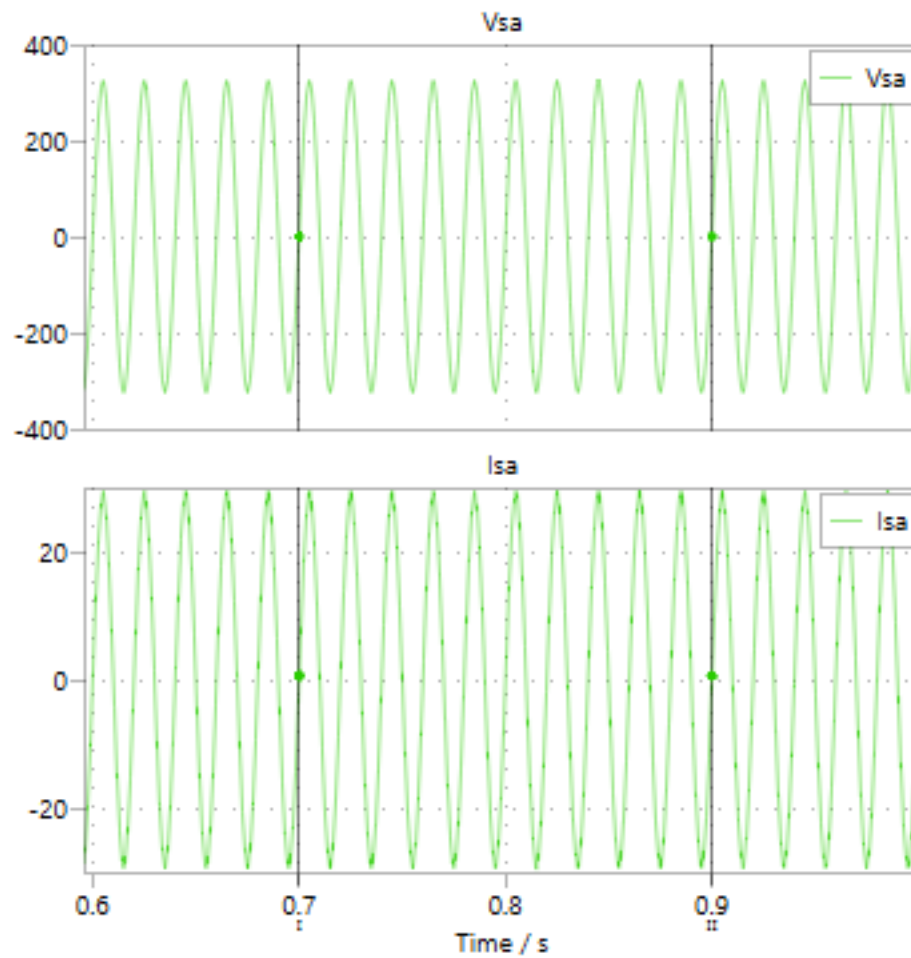
a.



Name	Cursor 1	Cursor 2	RMS
Time	0.7	0.9	
✓ Vsa	<input checked="" type="checkbox"/>		
✓ 	<input checked="" type="checkbox"/> -7.15872e-12	<input checked="" type="checkbox"/> -1.27269e-12	229.785
✓ Isa	<input checked="" type="checkbox"/>		
✓ 	<input checked="" type="checkbox"/> 0.660907	<input checked="" type="checkbox"/> 0.660907	20.3121

No change in fundamental RMS source current value with increase in filter inductance.


b.

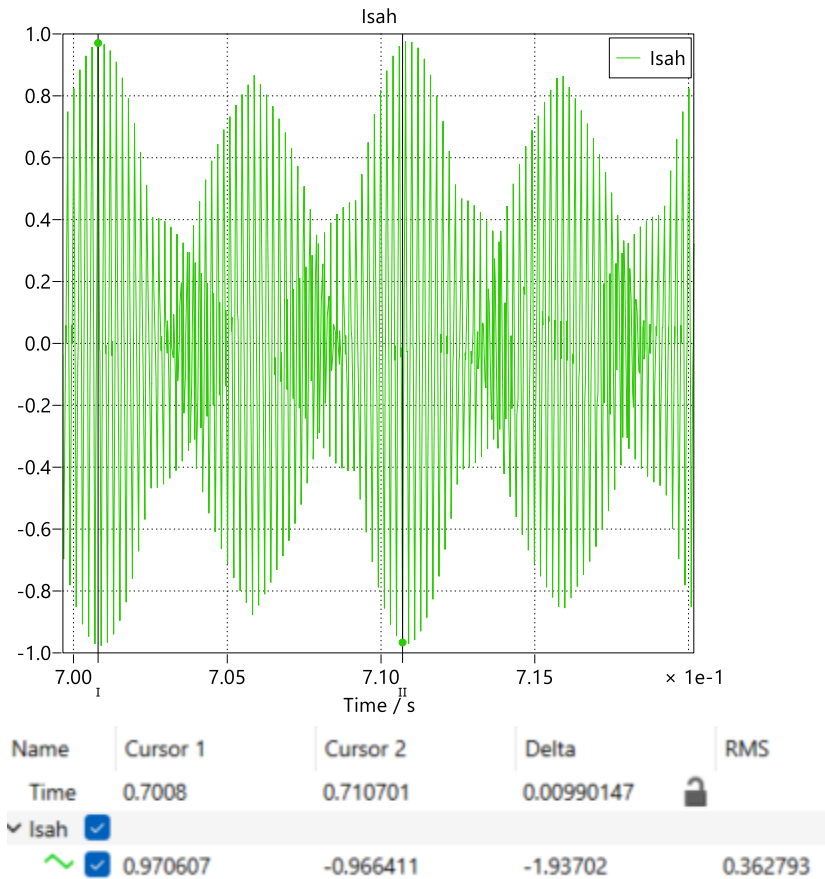

The peak-peak ripple current is 1.93702 A which is almost half of the peakpeak ripple current with 5 mH filter inductance. The increased inductance helps in reducing the ripple in source currents.


c.

Name	Cursor 1	Cursor 2	Delta	RMS
Time	0.72	0.720858	0.00085807	
Vsa & Vconv_a1				
Vsa	-2.86537e-12	86.544	86.544	50.2102
Vconv_a1	-90.2296	-0.426998	89.8026	52.4737

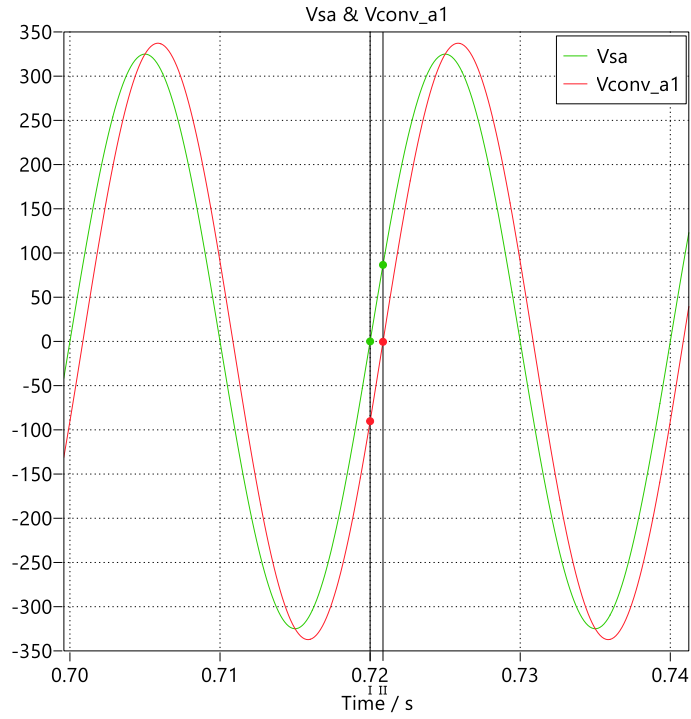

V_{conv1} lags V_s by a time of 0.85807 ms and its equivalent angle in degrees is 14.44526 which is almost double that of with 5 mH filter inductance.

d.

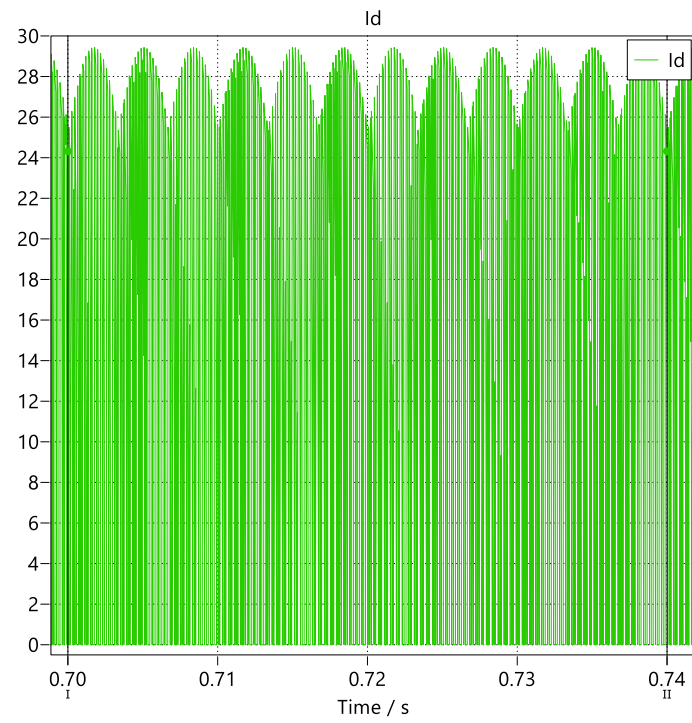

Name	Cursor 1	Cursor 2	Mear
Time	0.7	0.74	
✓ Id	<input checked="" type="checkbox"/>		
 <input checked="" type="checkbox"/>	24.3152	24.3152	20