

Module 6

Current-Sourced Converters

Content

- Current-sourced PWM rectifier
- Current-sourced PWM inverter
- Current-sourced vs voltage-sourced ac-ac frequency converter

Learning outcomes of the module

After the module, you will be able to:

- understand how current-sourced PWM rectifiers and inverters operate
- understand the difference between voltage- and current sourced converters

Current-type PWM rectifier

- Large smoothing inductance on the dc-side
 - Ideally perfect dc
 - Is an energy storage too
 - Requires continuous current path
- Dc-current is not changing polarity, dc-voltage can
 - Power can flow in both directions
- Very similar to line-commutated six-pulse thyristor bridge, except turn-on, turn-off devices (IGBT) and use of PWM instead of phase-shift modulation
- Converter has two changeover switches (SA, SB, SC) and (SA', SB' and SC')
 - each with three positions or poles
 - one of the poles has to be closed, otherwise there would not be a path for the load current i_o
 - $3 \times 3 = 9$ combinations for the conducting switches (see next slide)

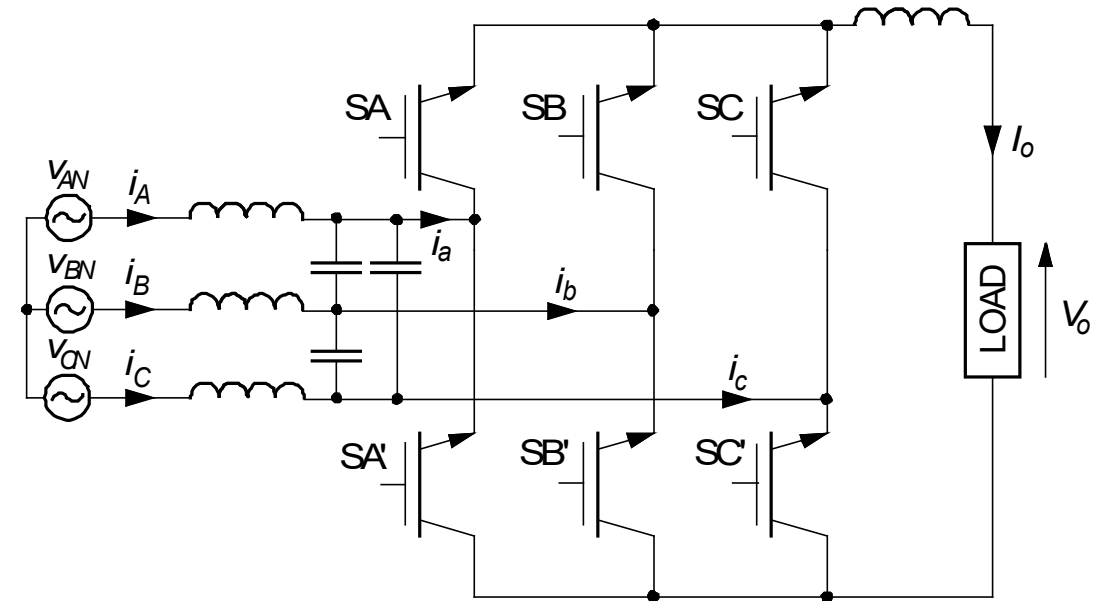


Fig. 4.45

Switching variables $a, b, c, a', b',$ and c' of switches SA through SC' must satisfy the condition

$$a + b + c = a' + b' + c' = 1.$$

It can be seen that the above condition limits the number of allowable states of the rectifier to 9, namely:

state 1: $a = b' = 1$ (conducting switches: SA & SB'),

state 2: $a = c' = 1$ (conducting switches: SA & SC'),

state 3: $b = c' = 1$ (conducting switches: SB & SC'),

state 4: $b = a' = 1$ (conducting switches: SB & SA'),

state 5: $c = a' = 1$ (conducting switches: SC & SA'),

state 6: $c = b' = 1$ (conducting switches: SC & SB'),

state 7: $a = a' = 1$ (conducting switches: SA & SA'), switches in the same phase conduct

state 8: $b = b' = 1$ (conducting switches: SB & SB'), switches in the same phase conduct

state 9: $c = c' = 1$ (conducting switches: SC & SC'), switches in the same phase conduct

E.g. in state 1, currents $i_A, i_B,$ and i_C equal $I_o, -I_o,$ and 0, respectively. Thus, the space vector of input currents in this state is

$$\vec{\mathcal{F}}_s = \mathcal{F}_{as} + \mathcal{F}_{bs}e^{j120^\circ} + \mathcal{F}_{cs}e^{j240^\circ} \qquad \vec{I}_1 = \frac{3}{2}I_o - j\frac{\sqrt{3}}{2}I_o.$$

Current vectors associated with the remaining states can be determined similarly. States 7, 8, and 9 produce zero vectors of input currents:

$$\vec{I}_7 = \vec{I}_8 = \vec{I}_9 = 0.$$

Reference current vector in the vector space of input currents of a current-type PWM rectifier

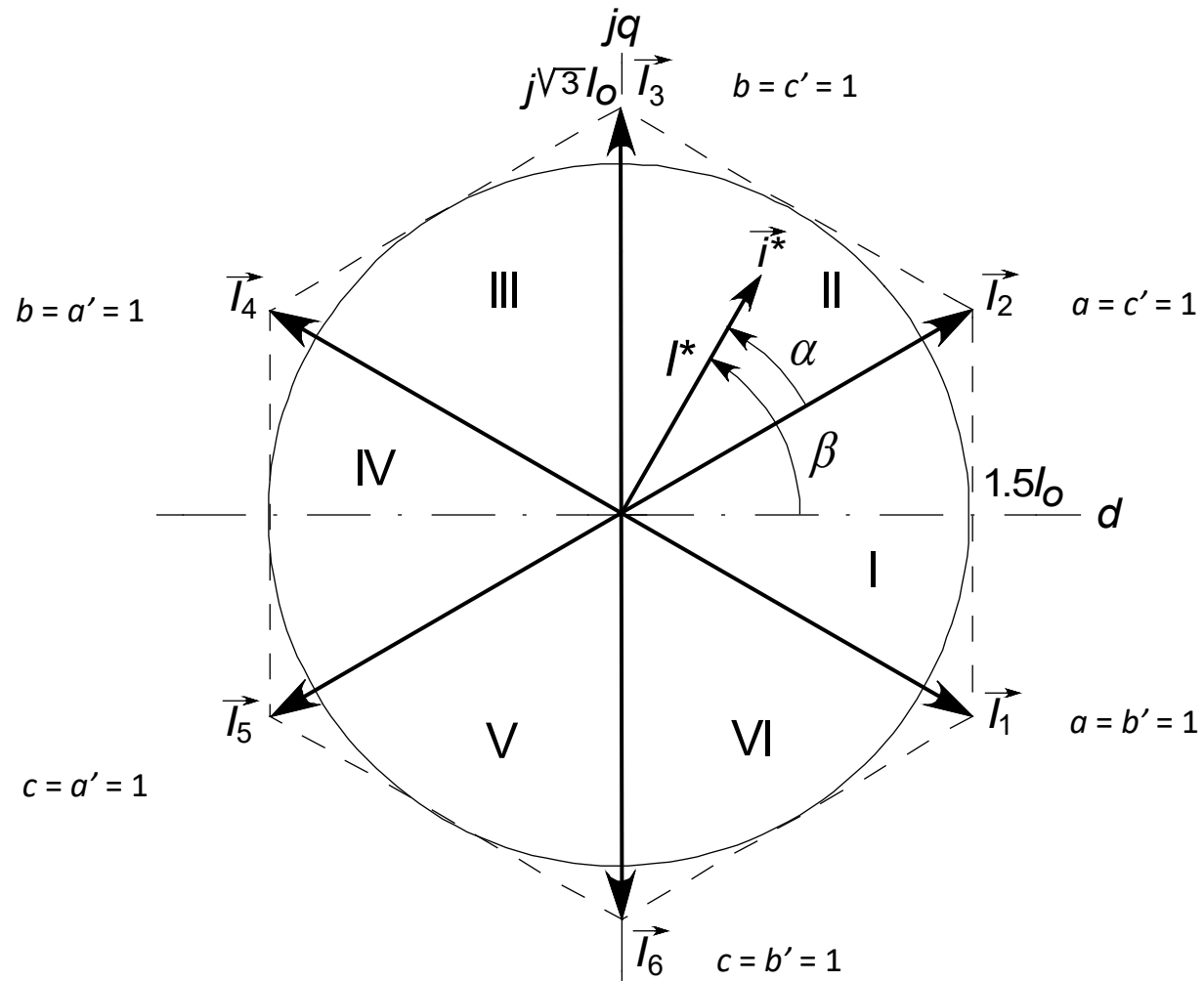


Fig. 4.46

Control scheme of a current-type PWM rectifier



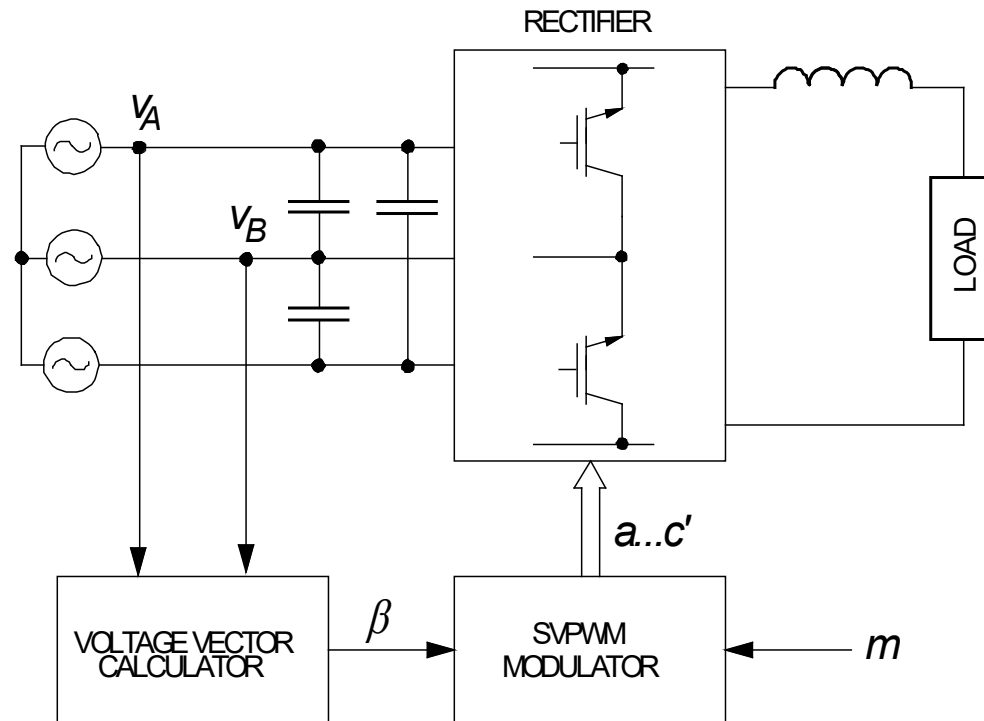


Fig. 4.48

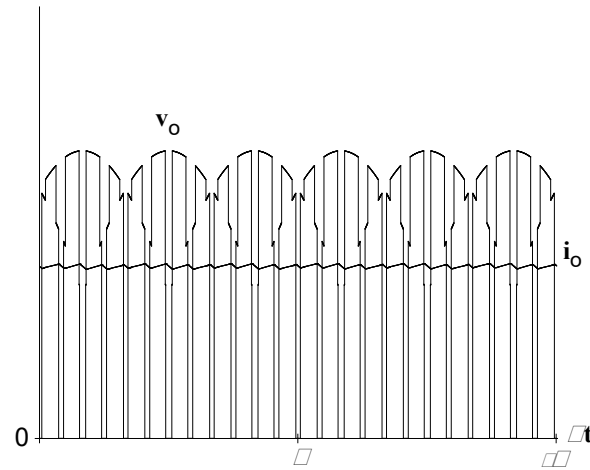Waveforms of output voltage and current in a current-type PWM rectifier:
(a) $m = 0.75$, (b) $m = 0.35$ ($f_{sw}/f_o = 24$, RLE load)




(a)

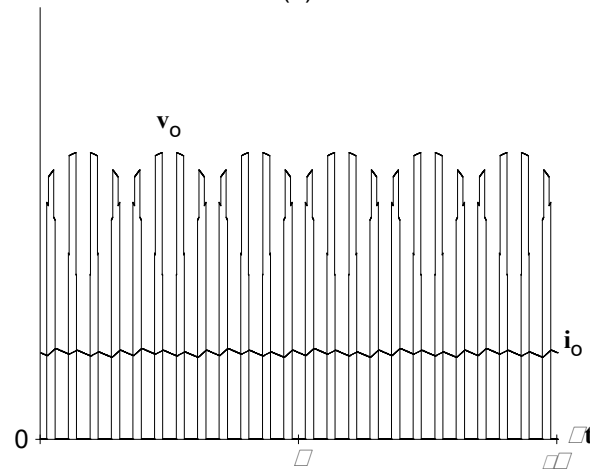


(b)

Fig. 4.49

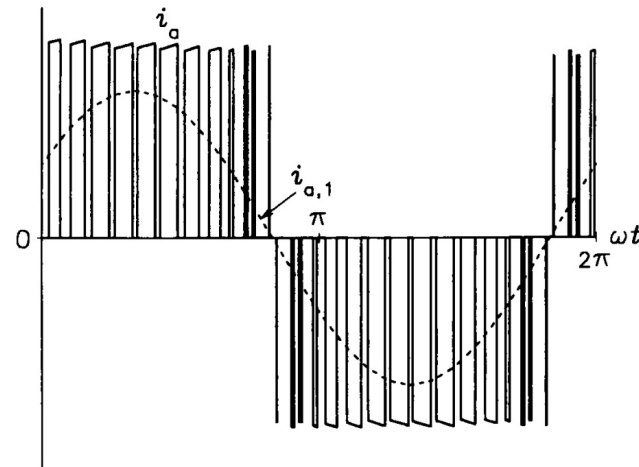Waveforms of the input current and its fundamental in a current-type PWM rectifier:
 (a) $m = 0.75$, (b) $m = 0.35$ ($f_{sw}/f_o = 24$, RLE load)



(a)

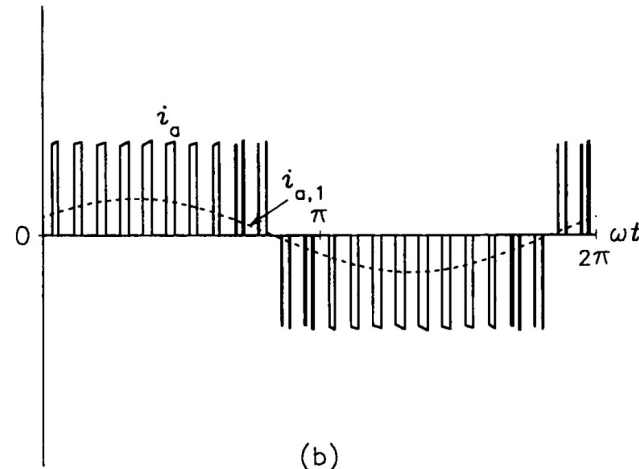

(b)

Fig. 4.50

Waveforms of (a) output voltage and current,
 (b) input current and its fundamental
 in a current-type PWM rectifier in the **inverter mode**

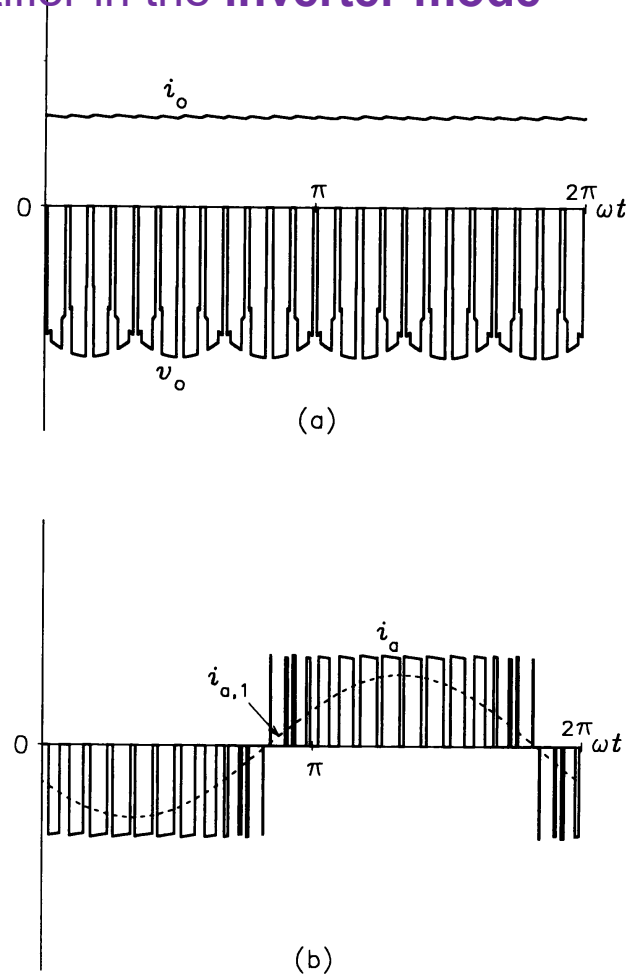


Fig. 4.51

CSI, Current Source Inverter

Current-source inverter supplied from a controlled rectifier

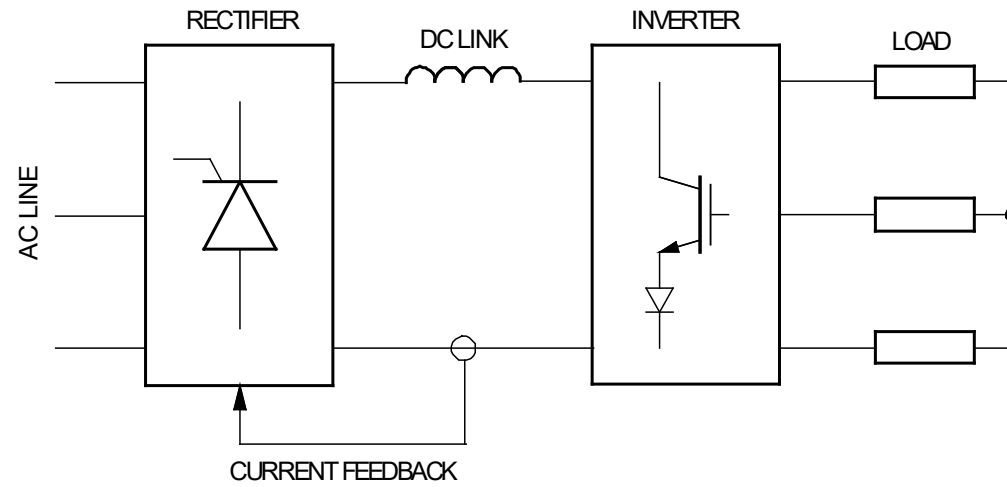


Fig. 7.43

Three-phase current-source inverter

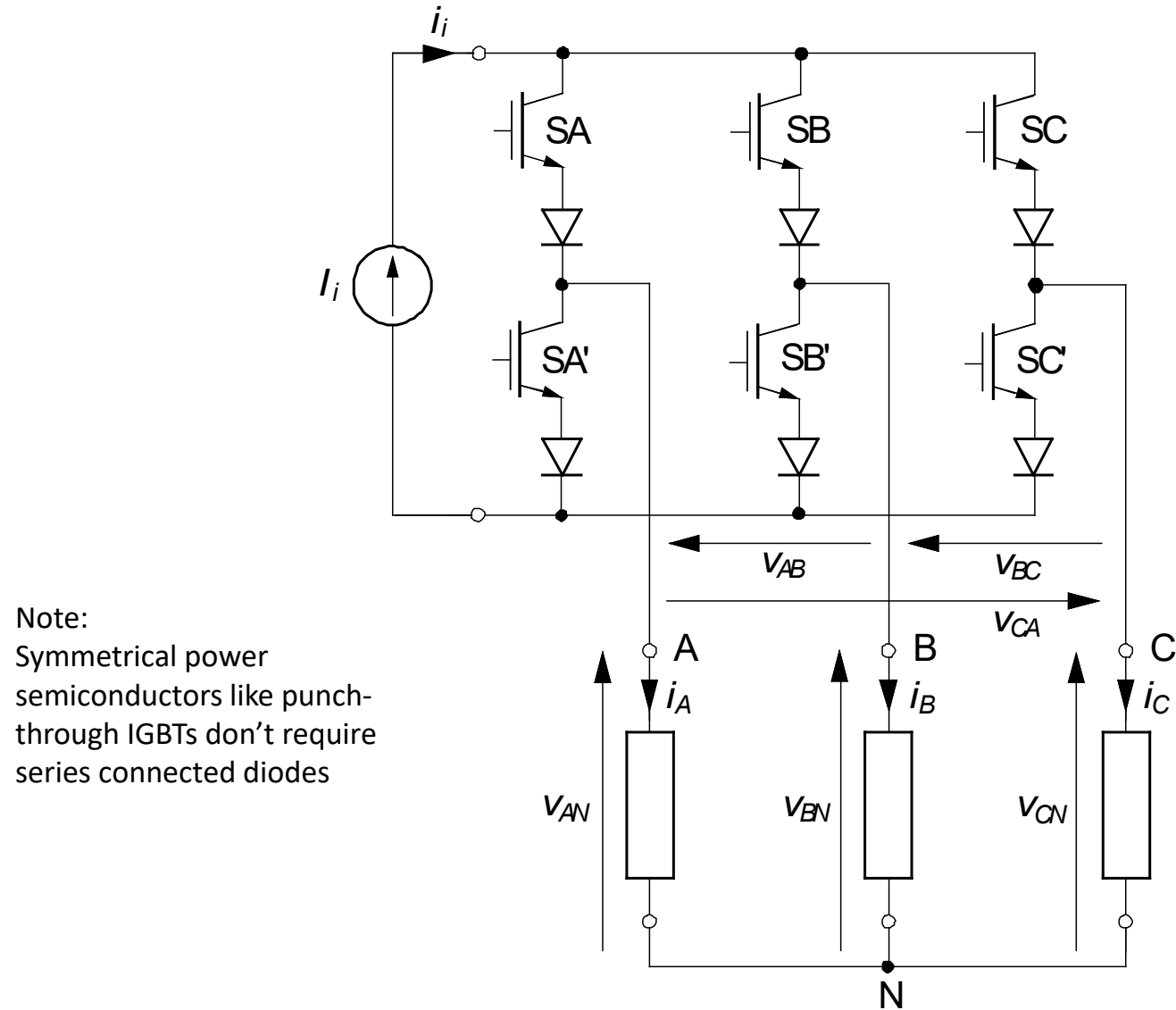


Fig. 7.44

Switching variables in a three-phase CSI in the square-wave mode

- Same idea as in Current Sourced Rectifier
- a, b or c needs to conduct the positive dc-current
- a', b' or c' needs to conduct the current back to dc minus

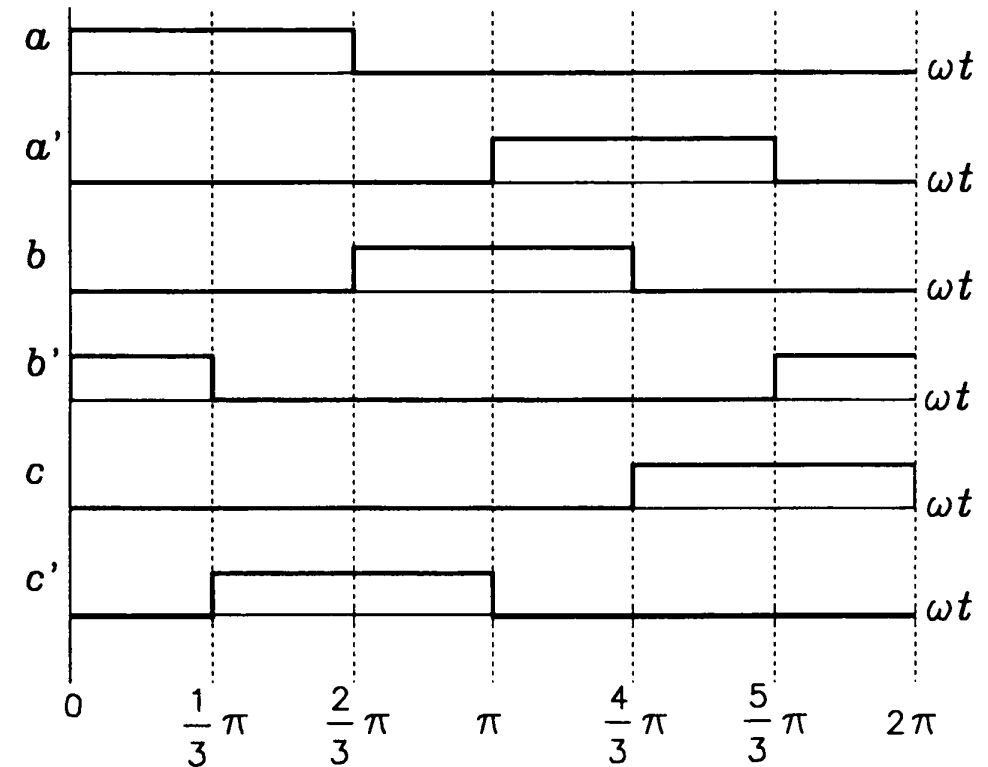


Fig. 7.45

Idealized waveforms of output currents in a three-phase CSI in the square-wave mode

Wye-connected load

$$\begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} a - d' \\ b - b' \\ c - c' \end{bmatrix} I_i$$

Delta-connected load

$$\begin{bmatrix} i_{AB} \\ i_{BC} \\ i_{CA} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix}$$

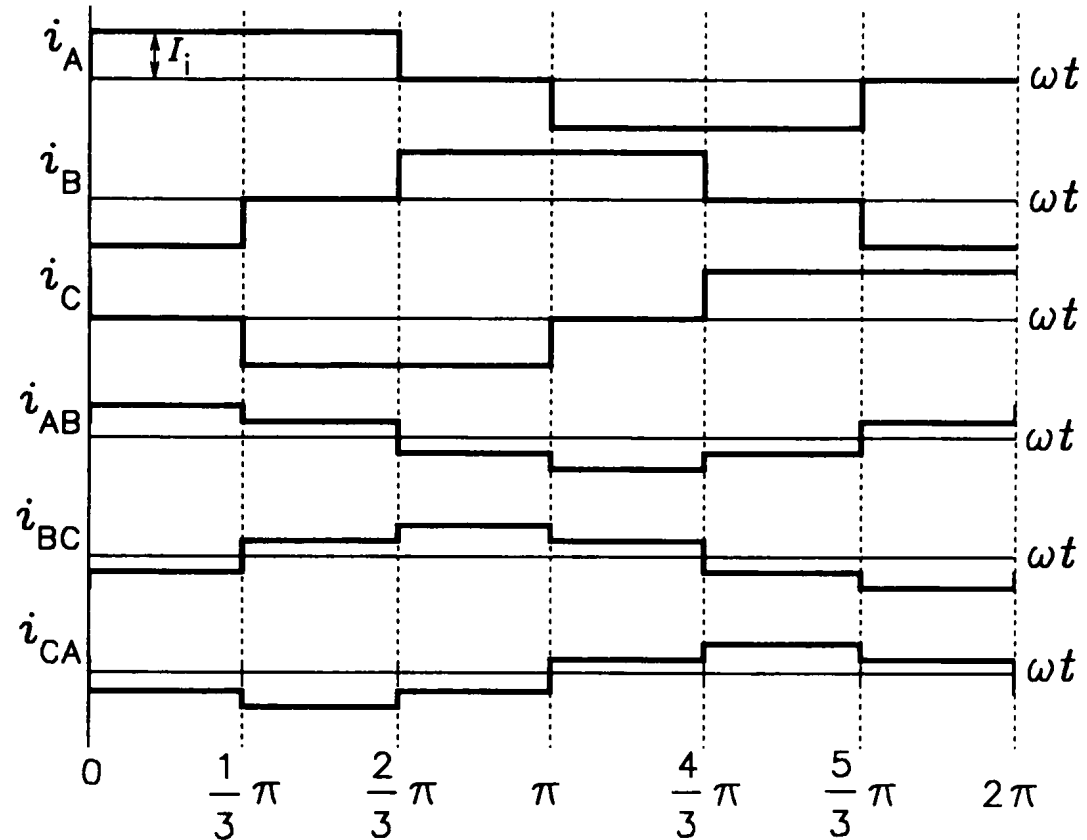


Fig. 7.46

Waveforms of output voltage and current in a three-phase CSI in the square-wave mode:

- Load current is given by the CSI
- In an inductive load current cannot change instantaneously => induced voltage spike in voltage waveforms

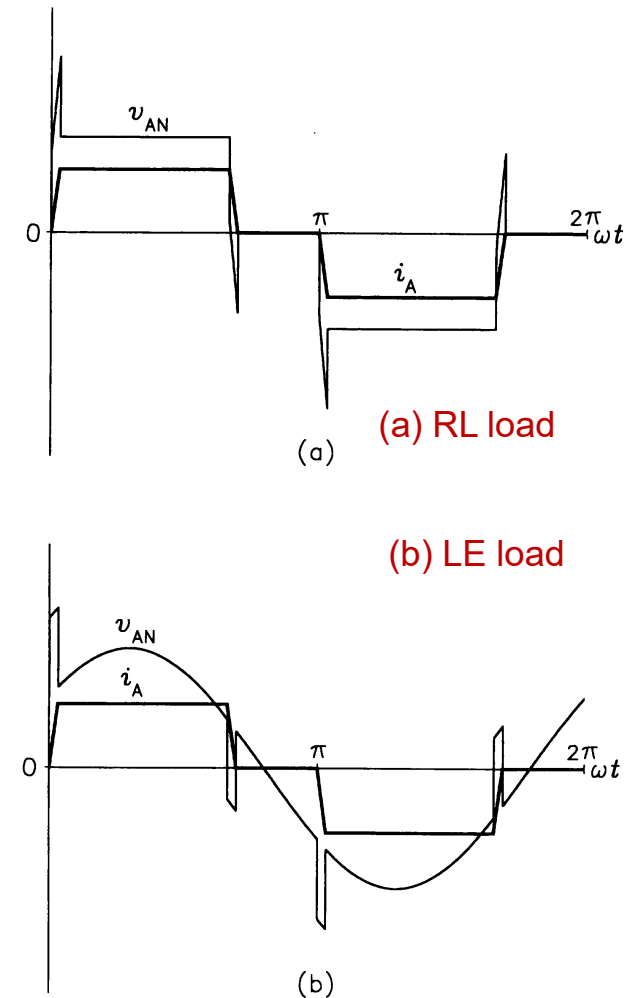


Fig. 7.47

Carrier-comparison method for the PWM CSI

- Pulse width modulation can be used to reduce the fundamental component of current
- Directly same PWM methods as for VSI cannot be used
- In CSI PWM must guarantee that the dc bus current is always connected to the load

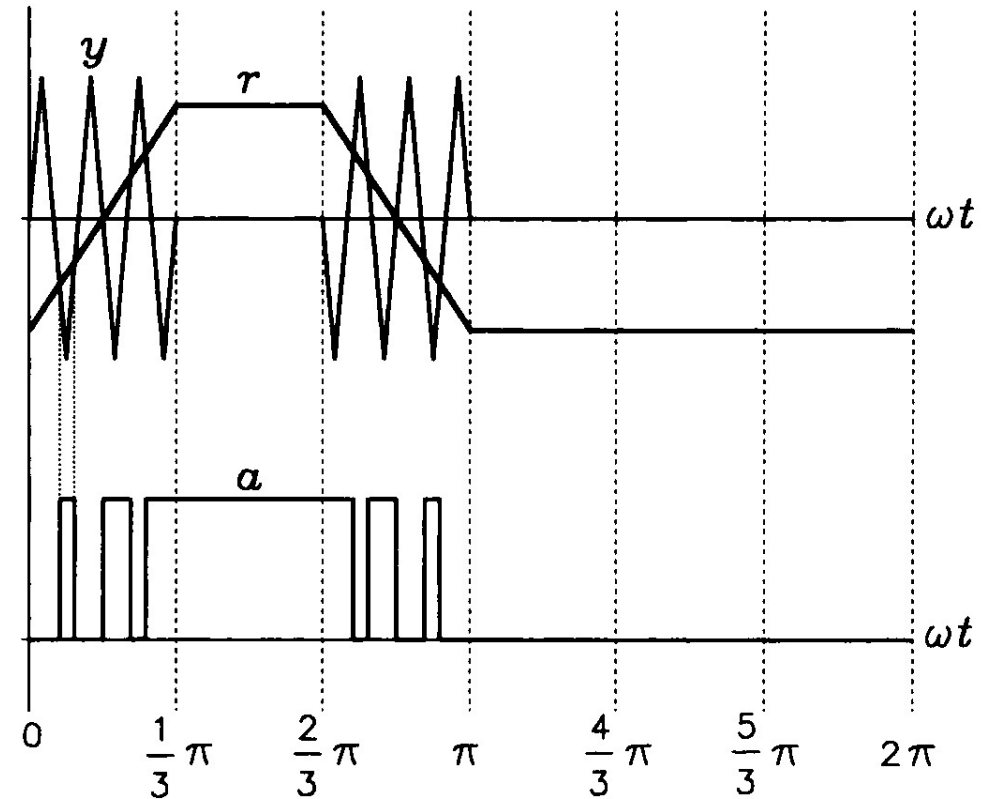


Fig. 7.49

Waveforms of the output current, capacitor current, and output voltage in a three-phase PWM CSI
(wye-connected RL load, $P = 9$)

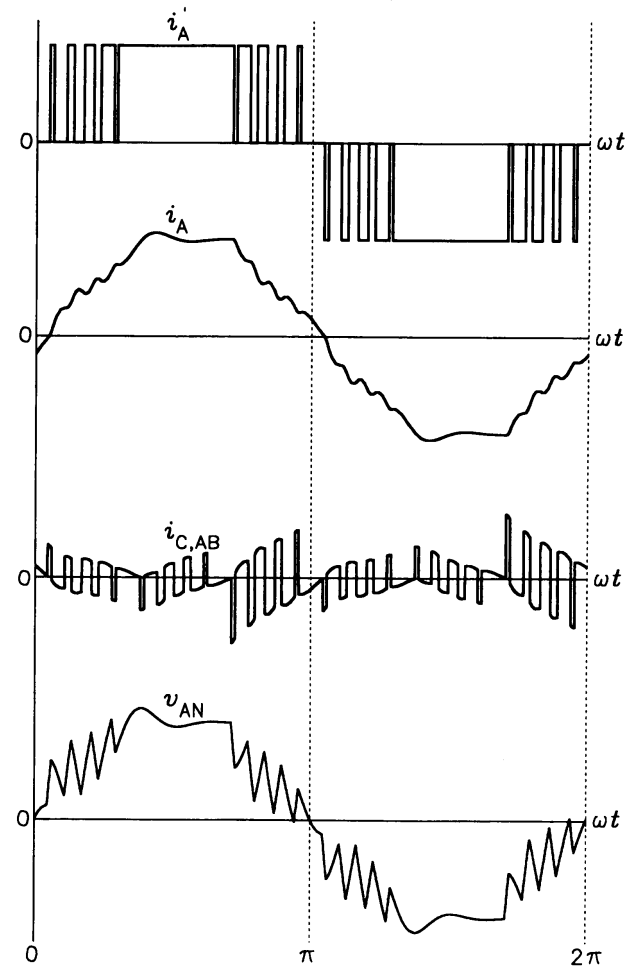


Fig. 7.51

Three-phase PWM current-source converter

- Thyristor converter is used as a rectifier
- It can also feed power to the ac grid when dc voltage is reversed
- Amplitude of the dc link current is adjusted with the rectifier


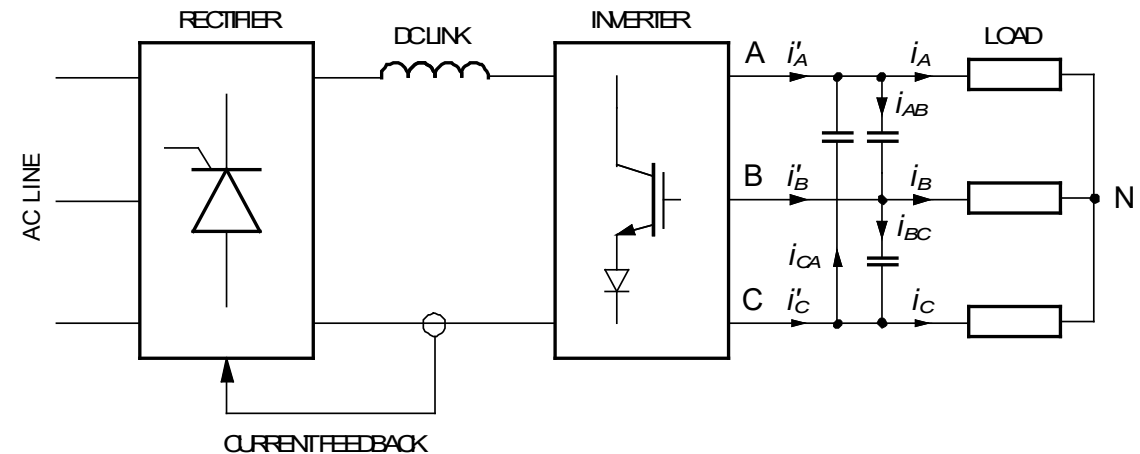
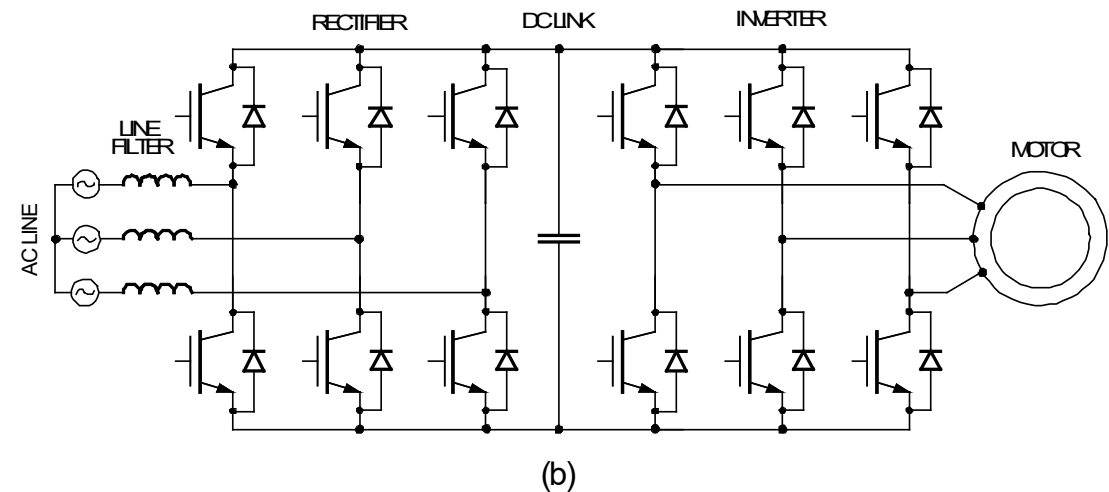


Fig. 7.48

PWM rectifier-inverter cascades for bidirectional power flow in ac motor drives:

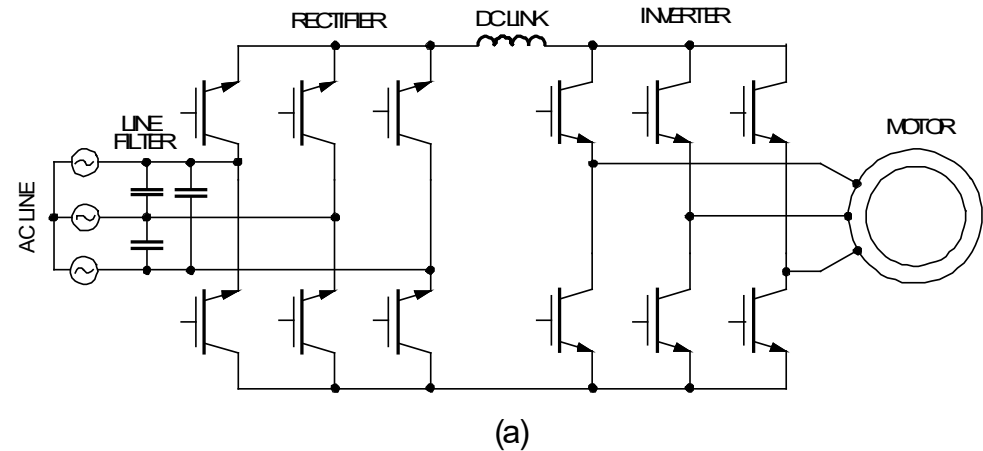- (a) current-type rectifier, inductive dc link, and current-source inverter,
- (b) voltage-type-rectifier, capacitive dc link, and voltage-source inverter



Summary of the module

- Current-type converters have a current source in the dc-bus and in practice it is a large enough series connected inductance.
- Current-type converters can be used as inverters and rectifiers in a same way as voltage-type converters.
- PWM can be used in current-type converters but it is not similar to PWM VSI. In current-type converters a bath for the dc-bus current needs to be guaranteed. In VSI short-circuit of the dc-bus needs to be avoided.